

Analysis and Design of Analog Integrated Circuits
Lecture 15

Mismatch and Nonlinearity


Michael H. Perrott

March 21, 2012

Copyright © 2012 by Michael H. Perrott


All rights reserved.

A Closer Look at Differential Pairs

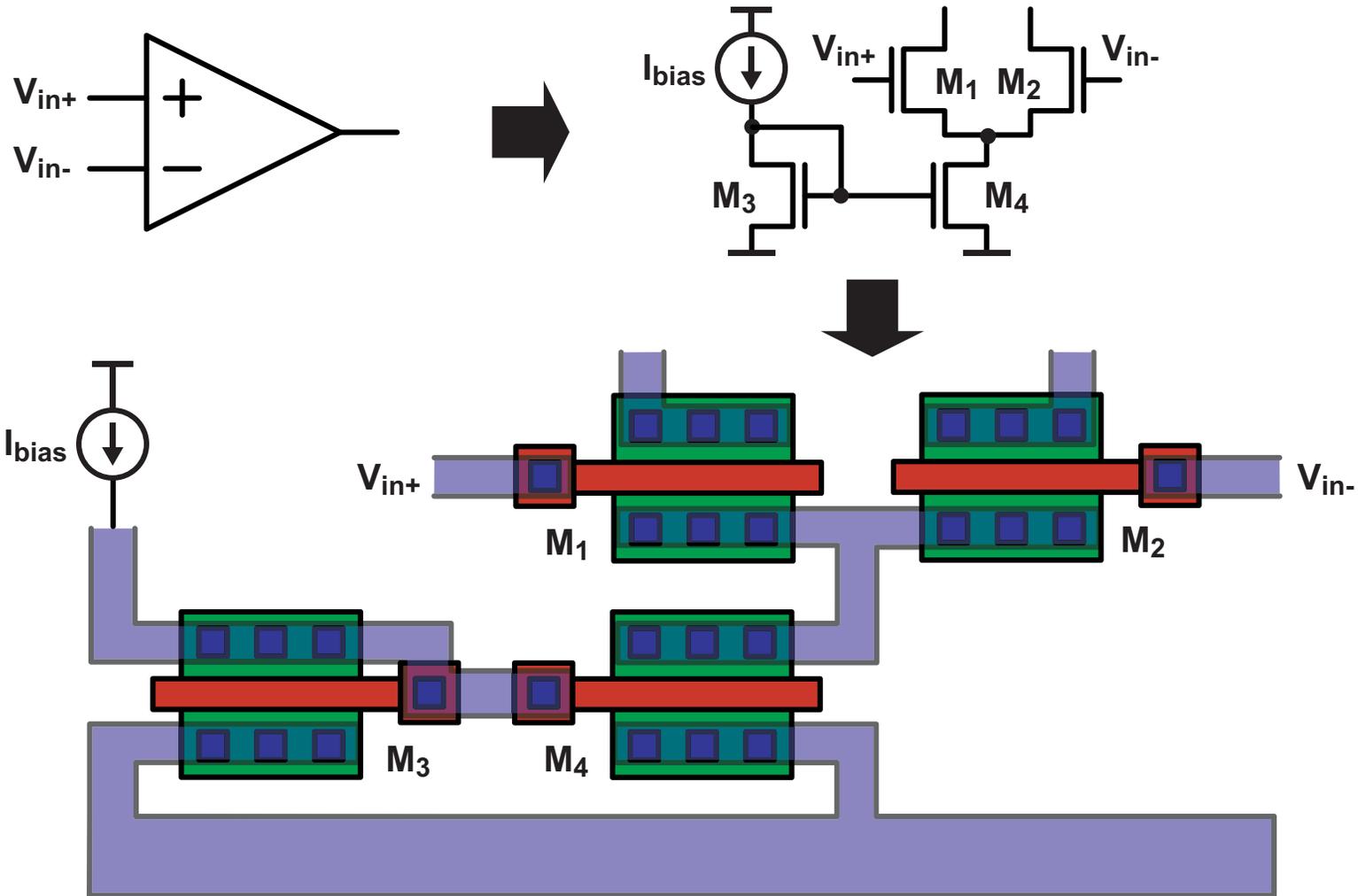

- **Fabrication of devices comes with variation**
 - Width, length, and $\mu_n C_{ox}$ mismatch between devices
 - Threshold voltage mismatch between devices

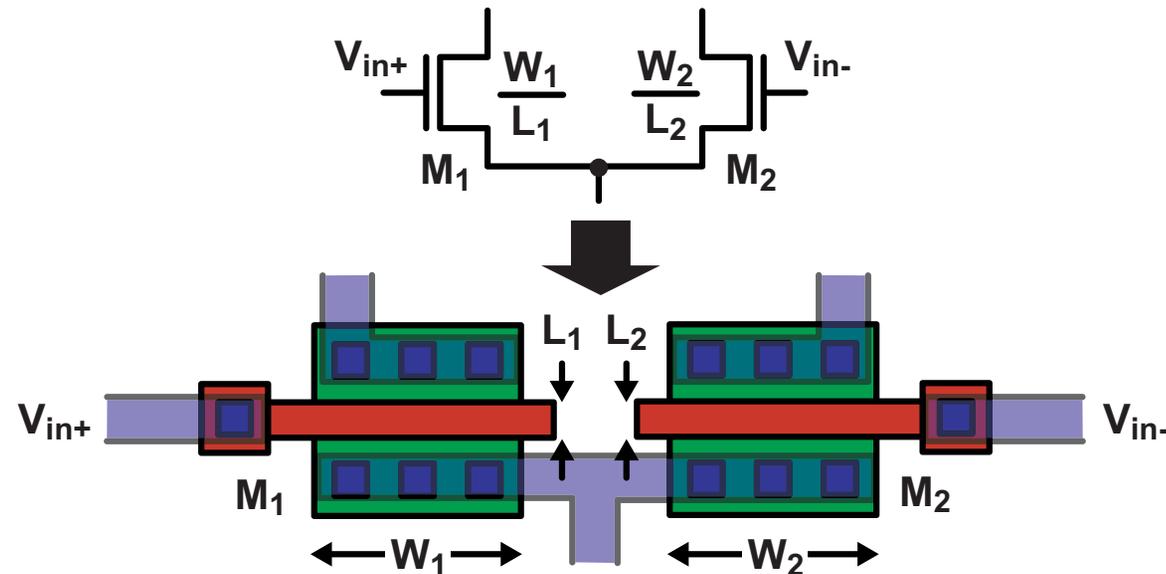Modeling the Impact of Mismatch in MOS Devices



- Compare the drain current of devices in saturation:

- Assume M_1 has current:


$$I_{D1} \approx \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{gs} - V_{TH})^2$$

- Assume that M_2 is mismatched to M_1 :

$$I_{D2} \approx \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} + \Delta \frac{W}{L} \right) (V_{gs} - (V_{TH} + \Delta V_{TH}))^2$$


- Note that $\mu_n C_{ox}$ mismatch is lumped into $\Delta(W/L)$

Key Impact of Mismatch

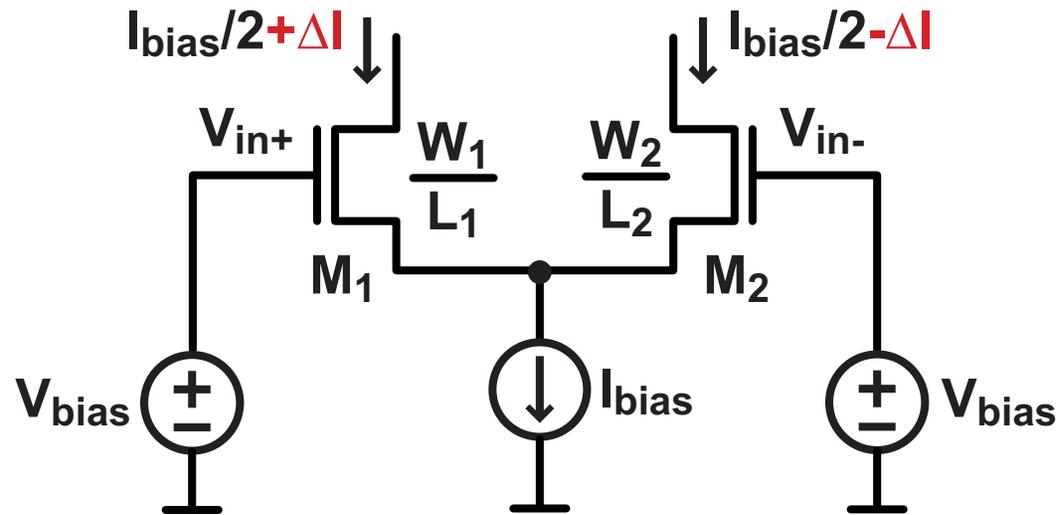


- Ideally, a differential pair will yield identical output currents assuming identical input voltages for V_{in+} and V_{in-}
- In the case of mismatch, the output currents will **NOT** be equal with equal input voltages

Mismatch-Induced Offset Voltage

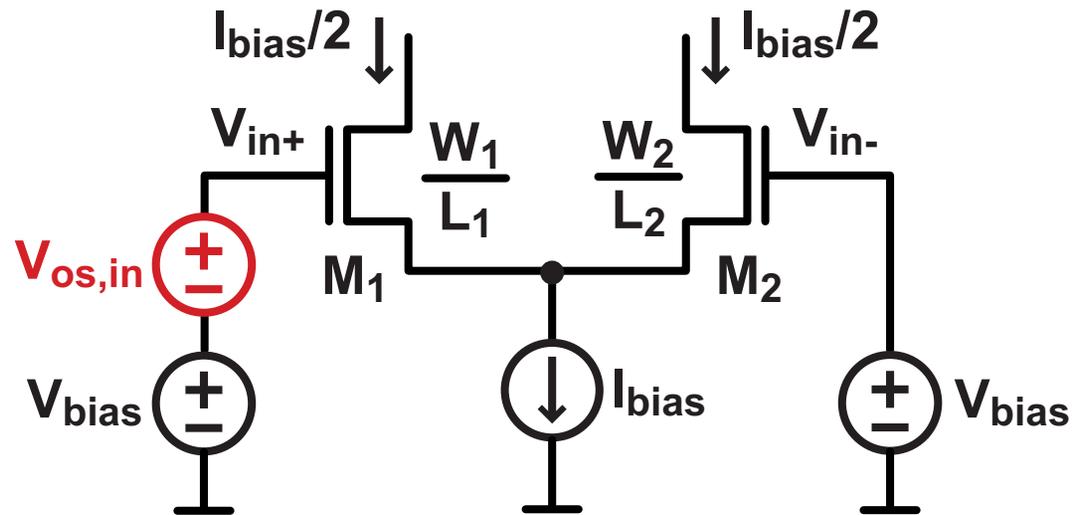

- Define input offset voltage of the differential pair as the input voltage difference required to achieve identical output currents from the differential pair
 - Higher mismatch leads to higher offset voltage

Mismatch Modeled as Random Variables

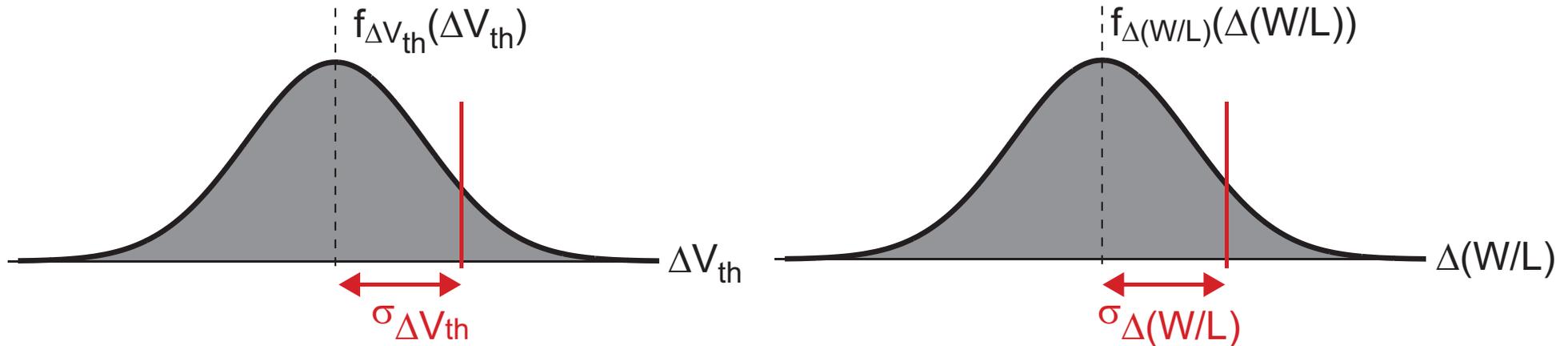


- We often assume a Gaussian PDF for the *random* portion of mismatch
 - The standard deviation of the PDF is the key metric that we often use to approximate the impact of mismatch

$$\Delta V_{TH} \approx \sigma_{\Delta V_{TH}} \quad \Delta \frac{W}{L} \approx \sigma_{\Delta \frac{W}{L}}$$

- Note that there is also a deterministic portion of mismatch called *systematic* mismatch
 - Systematic mismatch can often be avoided with proper design and layout techniques

Estimating Mismatch Parameters

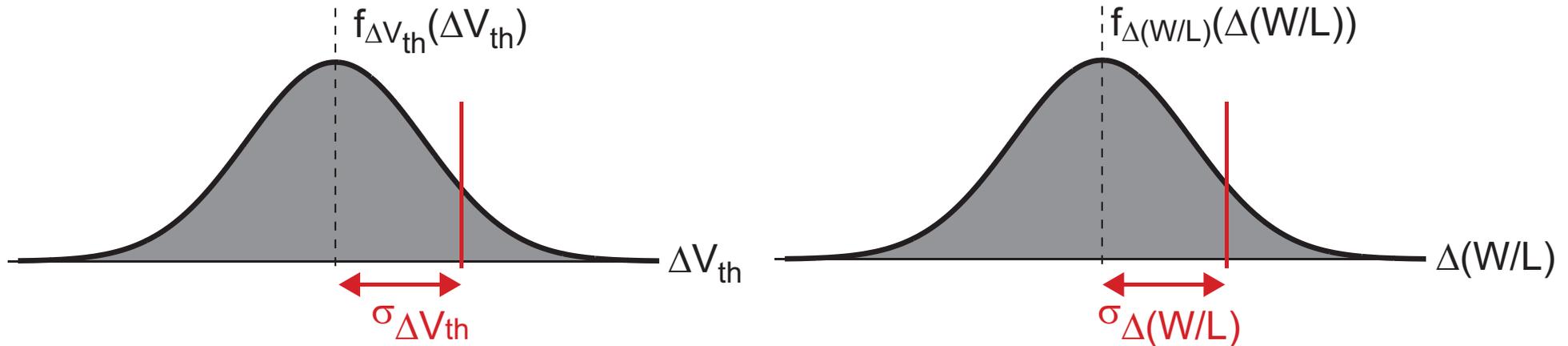

- **Mathematical and experimental investigation has revealed**

$$\sigma_{\Delta V_{TH}} \approx \frac{A_{V_{TH}}}{\sqrt{WL}} \qquad \sigma_{\Delta \frac{W}{L}} \approx \frac{A_K}{\sqrt{WL}}$$

- $A_{V_{TH}}$ and A_K are proportionality factors that are sometimes provided by fabrication reports and sometimes embedded within “Monte-Carlo” device models


Key insight: better matching achieved with larger devices

More Information on Mismatch

- **Marcel Pelgrom at NXP (formerly Philips) wrote the seminal papers on this topic**
 - **M.J.M. Pelgrom, A.C.J. Duinmaiger, A.P.G. Welbers, “Matching Properties of MOS Transistors,” IEEE J. Solid-State Circuits, vol. SC-24, pp. 1433-1439, Oct. 1989**
 - **M.J.M. Pelgrom, H.P. Tuinhout, M. Vertregt, “Transistor Matching in Analog CMOS Applications,” IEDM Dig. of Tech. Papers, pp. 34.1.1-34.1.4, Dec. 1998**

Nonlinearities in Amplifiers

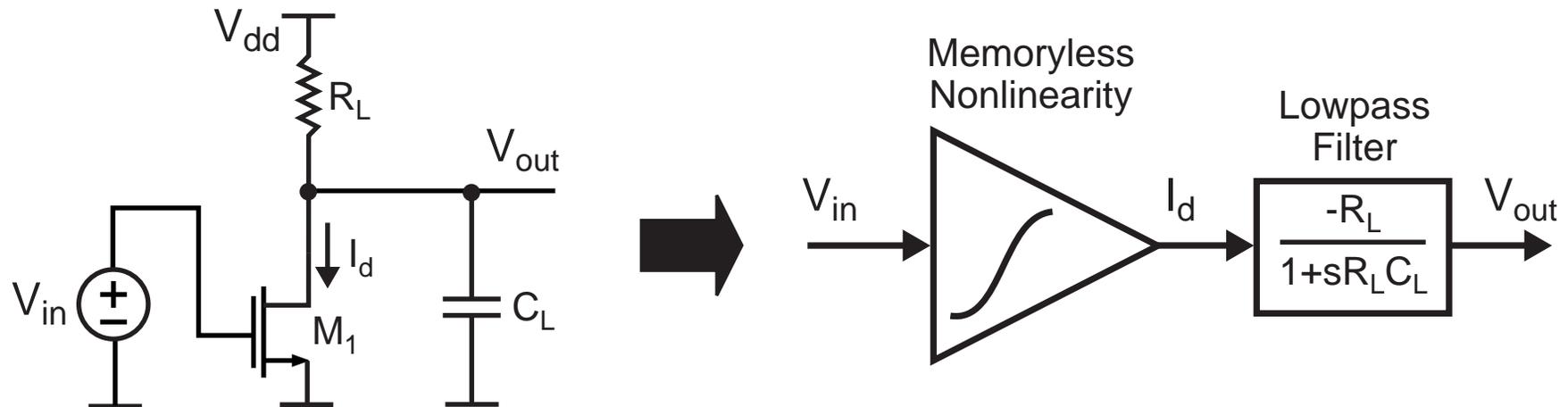- We can generally break up an amplifier into the cascade of a memoryless nonlinearity and an input and/or output transfer function




- Impact of nonlinearities with sine wave input
 - Causes harmonic distortion (i.e., creation of harmonics)
- Impact of nonlinearities with several sine wave inputs
 - Causes harmonic distortion for each input AND intermodulation products

Impact of nonlinearity often assessed based on issues related to communication system design

Analysis of Amplifier Nonlinearities

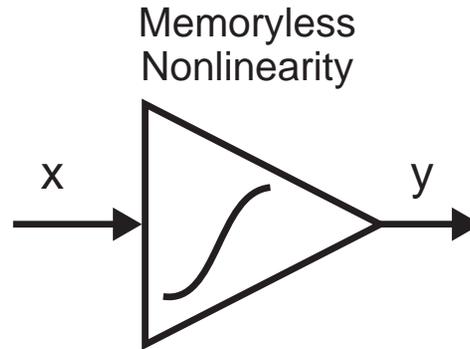- **Focus on memoryless nonlinearity block**
 - The impact of filtering can be added later



- **Model nonlinearity as a Taylor series expansion up to its third order term (assumes small signal variation)**

$$y(t) \approx c_0 + c_1x(t) + c_2x(t)^2 + c_3x(t)^3$$

- **For harmonic distortion, consider**

$$x(t) = A \cos(\omega t)$$

- **For intermodulation, consider**

$$x(t) = A(\cos(\omega_1 t) + \cos(\omega_2 t))$$

Harmonic Distortion

$$y(t) = c_0 + c_1x(t) + c_2x(t)^2 + c_3x(t)^3$$

$$\text{where } x(t) = A \cos wt$$

- **Substitute x(t) into polynomial expression**


$$y(t) - c_0 = c_1A \cos wt + c_2A^2 \cos^2 wt + c_3A^3 \cos^3 wt$$

$$= c_1A \cos wt + \frac{c_2A^2}{2}(1 + \cos 2wt) + \frac{c_3A^3}{4}(3 \cos wt + \cos 3wt)$$

$$= \frac{c_2A^2}{2} + \underbrace{\left(c_1A + \frac{3c_3A^3}{4} \right) \cos wt}_{\text{Fundamental}} + \underbrace{\frac{c_2A^2}{2} \cos 2wt + \frac{c_3A^3}{4} \cos 3wt}_{\text{Harmonics}}$$


- **Notice that each harmonic term, $\cos(nwt)$, has an amplitude that grows in proportion to A^n**
 - **Very small for small A, very large for large A**

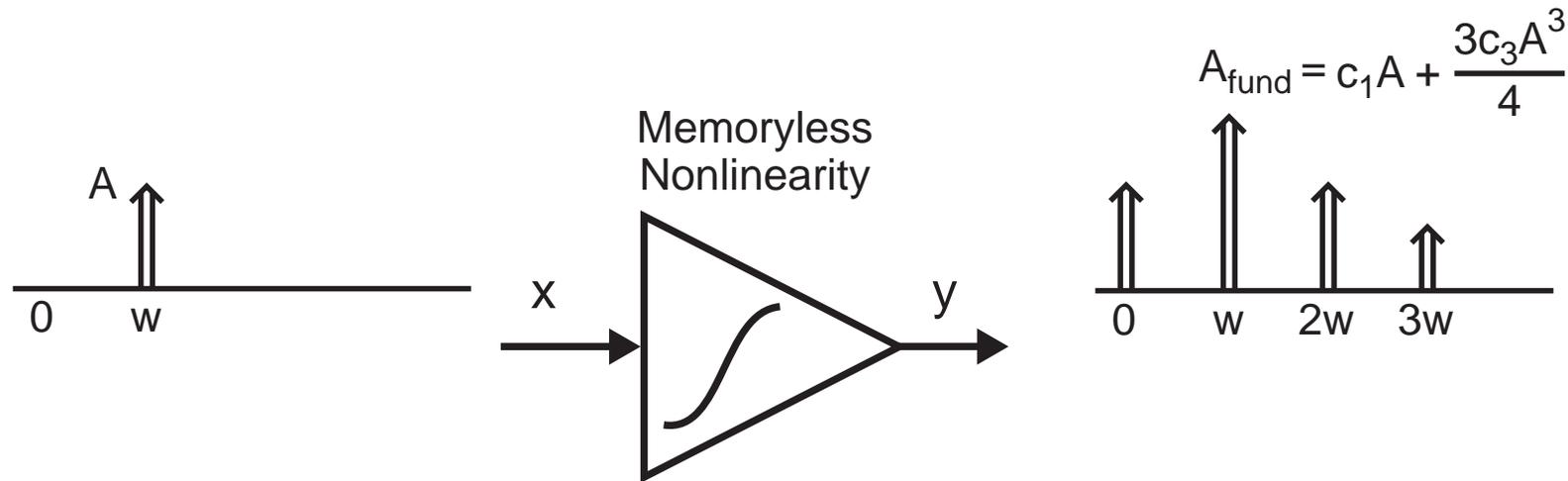Frequency Domain View of Harmonic Distortion




- **Harmonics cause “noise”**
 - Their impact depends highly on application
 - Low noise amplifiers (LNA) for wireless systems – typically not of consequence
 - Power amplifiers for wireless systems – can degrade spectral mask
 - Audio amp – depends on your listening preference!
- **Gain for fundamental component depends on input amplitude!**

1 dB Compression Point

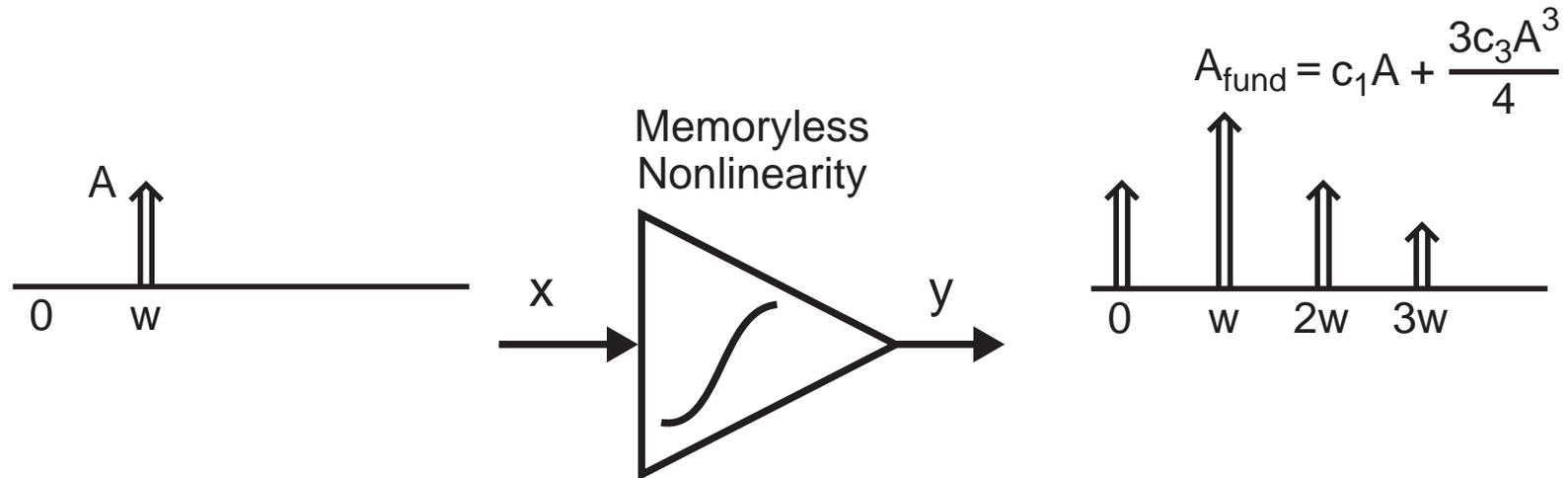

- **Definition: input signal level such that the small-signal gain drops by 1 dB**

- Input signal level is high!

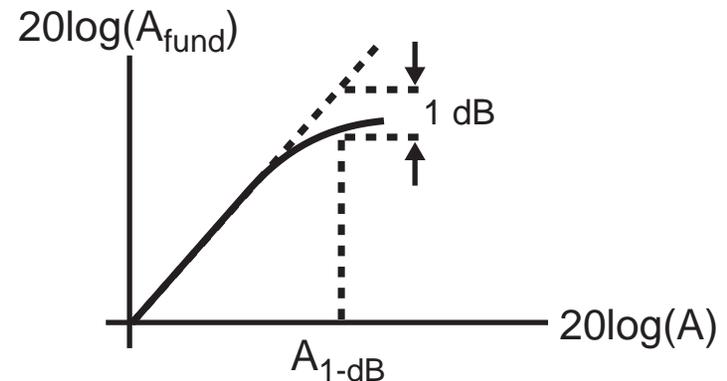

- **Typically calculated from simulation or measurement rather than analytically**
 - Analytical model must include many more terms in Taylor series to be accurate in this context

Harmonic Products with An Input of Two Sine Waves

$$y(t) = c_0 + c_1x(t) + c_2x(t)^2 + c_3x(t)^3$$

$$\text{where } x(t) = A(\cos w_1t + \cos w_2t)$$

- **DC and fundamental components**

$$\left(c_0 + c_2A^2 \right) + \left(\left(c_1A + \frac{9}{4}c_3A^3 \right) (\cos w_1t + \cos w_2t) \right)$$

- **Second and third harmonic terms**

$$\left(\frac{c_2A^2}{2} (\cos 2w_1t + \cos 2w_2t) \right) + \left(\frac{c_3A^3}{4} (\cos 3w_1t + \cos 3w_2t) \right)$$

- **Similar result as having an input with one sine wave**

- **But, we haven't yet considered cross terms!**

Intermodulation Products

$$y(t) = c_0 + c_1x(t) + c_2x(t)^2 + c_3x(t)^3$$

$$\text{where } x(t) = A(\cos w_1t + \cos w_2t)$$

- **Second-order intermodulation (IM2) products**


$$c_2A^2(\cos(w_1 + w_2)t + \cos(w_2 - w_1)t)$$

- **Third-order intermodulation (IM3) products**

$$\frac{3}{4}c_3A^3 \left(\cos(2w_1 + w_2)t + \cos(2w_1 - w_2)t \right. \\ \left. + \cos(2w_2 + w_1)t + \cos(2w_2 - w_1)t \right)$$


- **These are the troublesome ones for narrowband wireless systems**

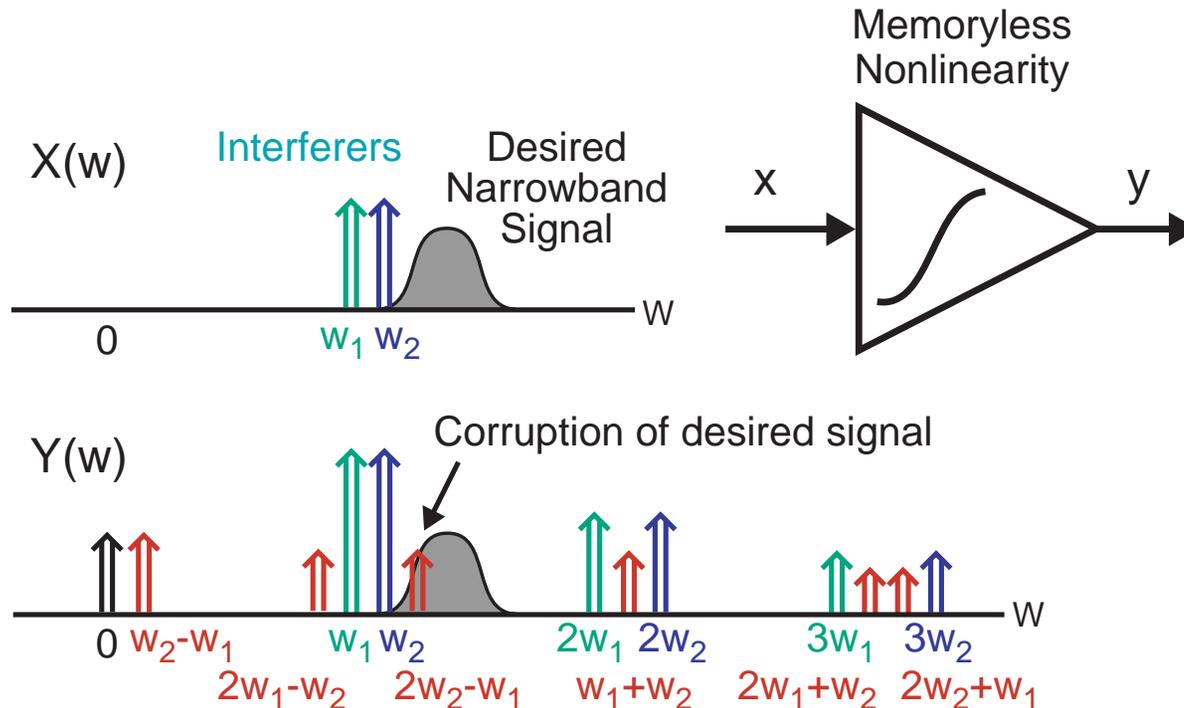Corruption of Narrowband Signals by Interferers



- **Wireless receivers must select a desired signal that is accompanied by interferers that are often much larger**
 - LNA nonlinearity causes the creation of harmonic and intermodulation products
 - Must remove interference and its products to retrieve desired signal

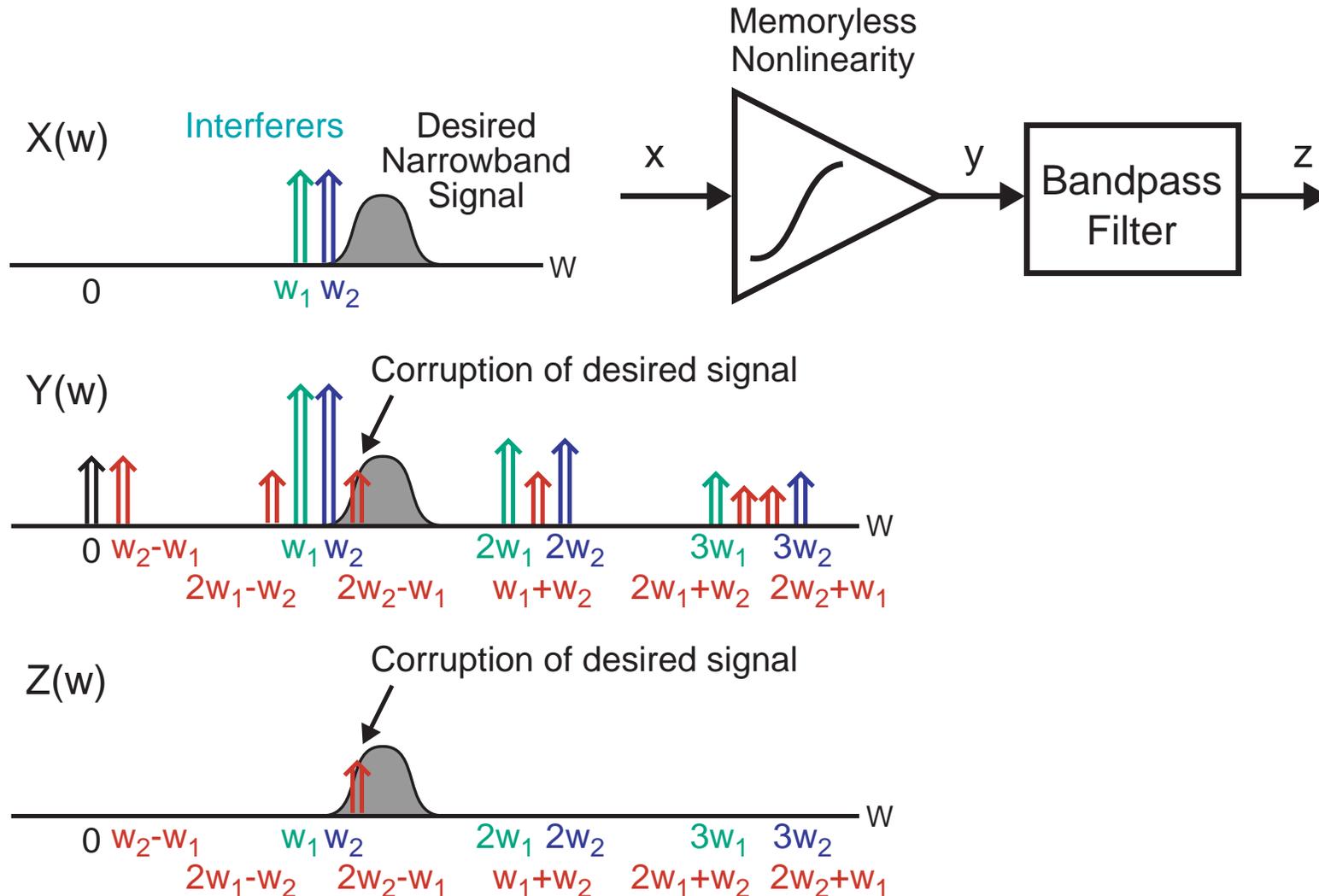Use Filtering to Remove Undesired Interference



- Ineffective for IM3 term that falls in the desired signal frequency band

Characterization of Intermodulation

- **Magnitude of third order products is set by c_3 and input signal amplitude (for small A)**

$$\frac{3}{4}c_3A^3 \left(\cos(2w_1 + w_2)t + \cos(2w_1 - w_2)t \right. \\ \left. + \cos(2w_2 + w_1)t + \cos(2w_2 - w_1)t \right)$$


- **Magnitude of first order term is set by c_1 and A (for small A)**

$$\left(c_1A + \frac{9}{4}c_3A^3 \right) (\cos w_1t + \cos w_2t) \approx c_1A (\cos w_1t + \cos w_2t)$$

- **Relative impact of intermodulation products can be calculated once we know A and the ratio of c_3 to c_1**
 - **Problem: it's often hard to extract the polynomial coefficients through direct DC measurements**
 - **Need an indirect way to measure the ratio of c_3 to c_1**

Two Tone Test

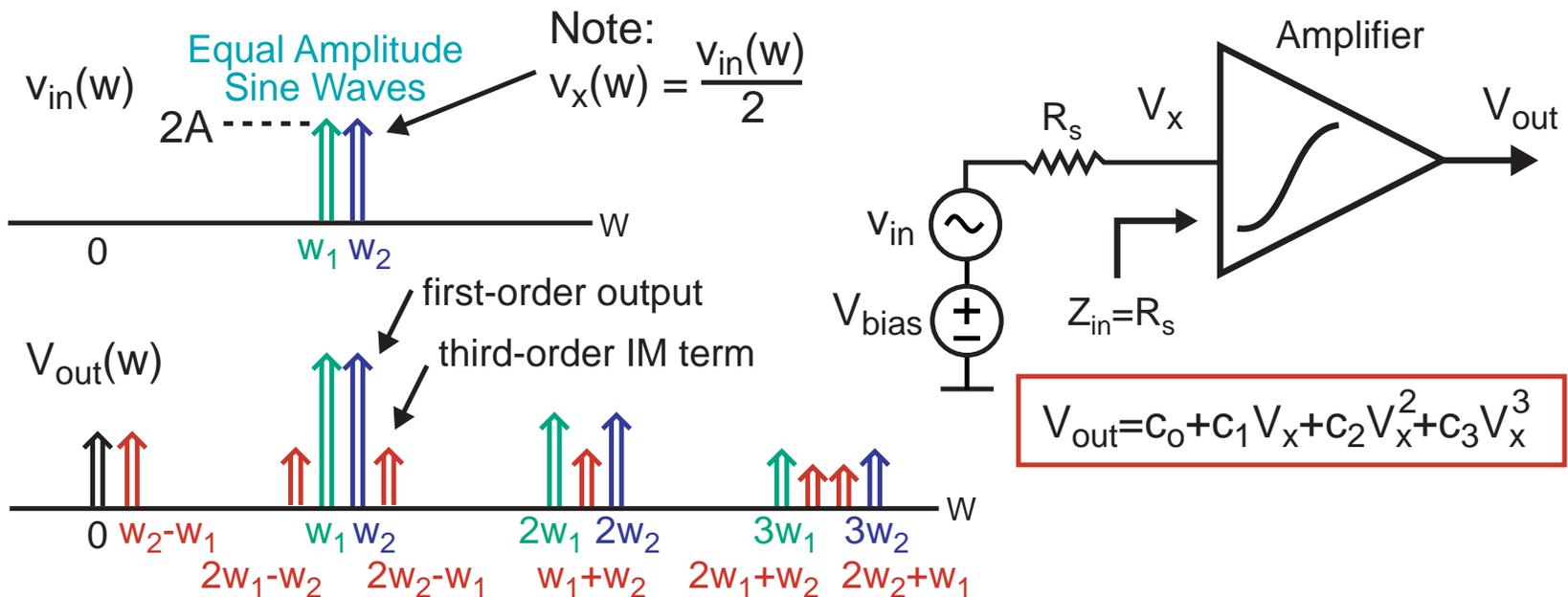
- Input the sum of two equal amplitude sine waves into the amplifier (assume Z_{in} of amplifier = R_s of source)



- On a spectrum analyzer, measure first order and third order terms as A is varied (A must remain small)
 - First order term will increase linearly
 - Third order IM term will increase as the cube of A

Input-Referred Third Order Intercept Point (IIP3)

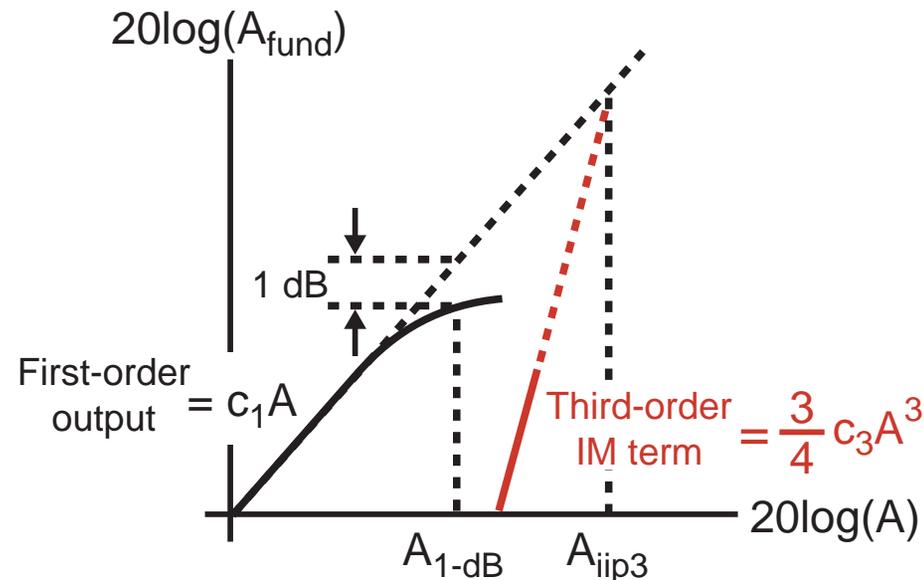- Plot the results of the two-tone test over a range of A (where A remains small) on a log scale (i.e., dB)
 - Extrapolate the results to find the intersection of the first and third order terms



- IIP3 defined as the input power at which the extrapolated lines intersect (higher value is better)
 - Note that IIP3 is a small signal parameter based on extrapolation, in contrast to the 1-dB compression point


Relationship between IIP3, c_1 and c_3

- Intersection point

$$|c_1 A| = \left| \frac{3}{4} c_3 A^3 \right|$$

- Solve for A (gives A_{iip3})

$$\Rightarrow A^2 = \frac{4}{3} \left| \frac{c_1}{c_3} \right| (V_p^2)$$

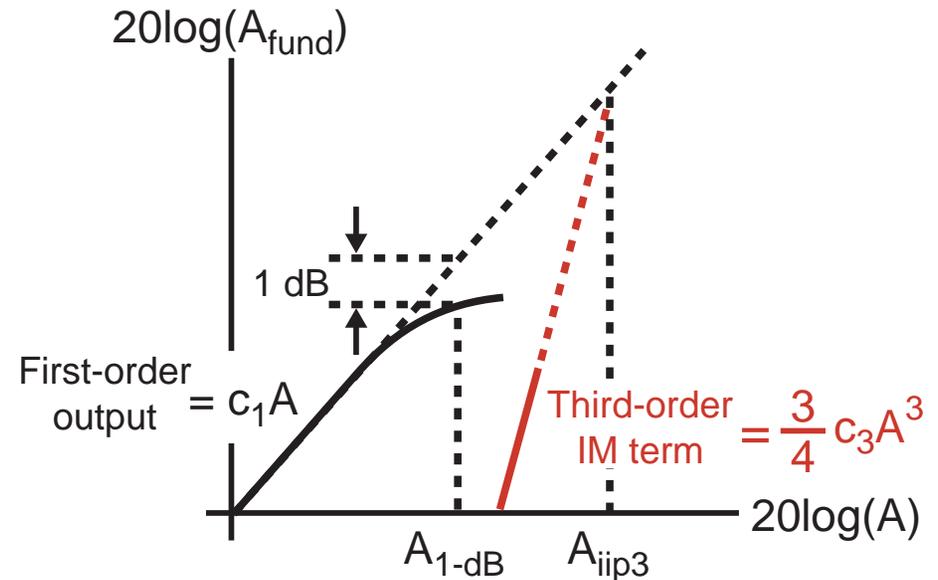

- Note that A corresponds to the peak value of the two cosine waves coming into the amplifier input node (V_x)
 - Would like to instead like to express IIP3 in terms of power

IIP3 Expressed in Terms of Power at Source

- IIP3 referenced to V_x (peak voltage)

$$A^2 = \frac{4}{3} \left| \frac{c_1}{c_3} \right| (V_p^2)$$

- IIP3 referenced to V_x (rms voltage)

$$A_{rms}^2 = \left(\frac{A}{\sqrt{2}} \right)^2 = \frac{2}{3} \left| \frac{c_1}{c_3} \right| (V_{rms}^2)$$


- Power across $Z_{in} = R_s$

$$\frac{A_{rms}^2}{R_s} = \frac{2}{3} \left| \frac{c_1}{c_3} \right| \frac{1}{R_s} \text{ (Watts)}$$

- Note: Power from v_{in}

$$2 \frac{A_{rms}^2}{R_s} = \frac{4}{3} \left| \frac{c_1}{c_3} \right| \frac{1}{R_s} \text{ (Watts)}$$


$$\Rightarrow IIP3(dBm) = 10 \log \left((10^3) \frac{2}{3} \left| \frac{c_1}{c_3} \right| \frac{1}{R_s} \right) \text{ (dBm)}$$

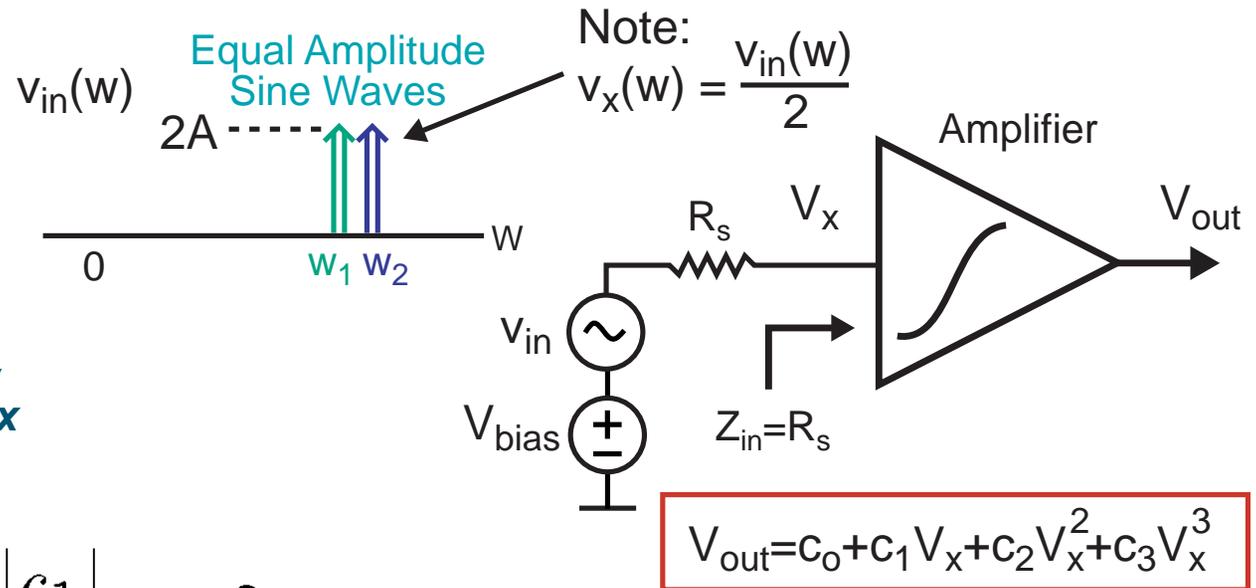

IIP3 as a Benchmark Specification

- **Since IIP3 is a convenient parameter to describe the level of third order nonlinearity in an amplifier, it is often quoted as a benchmark spec**
- **Measurement of IIP3 on a discrete amplifier would be done using the two-tone method described earlier**
 - **This is rarely done on integrated amplifiers due to poor access to the key nodes**
 - **Instead, for a radio receiver for instance, one would simply put in interferers and see how the receiver does**
 - **Note: performance in the presence of interferers is not just a function of the amplifier nonlinearity**
- **Calculation of IIP3 is most easily done using a Spice simulator**
 - **Two-tone method is not necessary – simply curve fit to a third order polynomial**

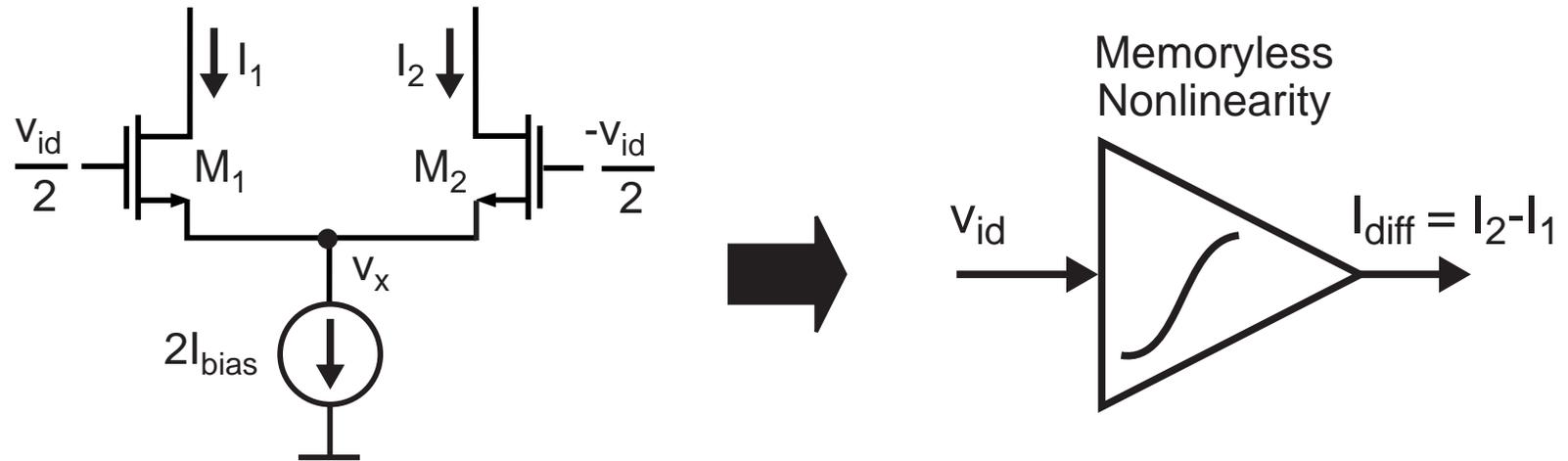Impact of Differential Amplifiers on Nonlinearity



- Assume v_x is approximately incremental ground

$$I_{diff} = c_0 + c_1 \frac{v_{id}}{2} + c_2 \left(\frac{v_{id}}{2} \right)^2 + c_3 \left(\frac{v_{id}}{2} \right)^3 - \left(c_0 + c_1 \frac{-v_{id}}{2} + c_2 \left(\frac{-v_{id}}{2} \right)^2 + c_3 \left(\frac{-v_{id}}{2} \right)^3 \right)$$

$$\Rightarrow I_{diff} = c_1 v_{id} + \frac{c_3}{4} v_{id}^3$$

- Second order term removed and IIP3 improved!

Summary

- **Mismatch between devices in differential pair circuits induces an effective offset voltage**
 - The value of the offset voltage is reduced by having large device dimensions
 - Fabrication reports or “Monte-Carlo” models provide the best approach to assessing the impact of mismatch
 - May not be available, which leads to guessing the impact
- **Nonlinearity is typically modeled as a third order polynomial**
 - Results in harmonic distortion and intermodulation
 - Third order component is often focused on in classical communication systems
 - Second order component is important for modern communication systems based on “direct conversion”
 - Differential pair offers some linearity advantages over single ended amplifiers