

***High Speed Communication Circuits and Systems***  
***Lecture 15***  
***Integer-N Frequency Synthesizers***


**Michael H. Perrott**

**March 31, 2004**

**Copyright © 2004 by Michael H. Perrott**


**All rights reserved.**
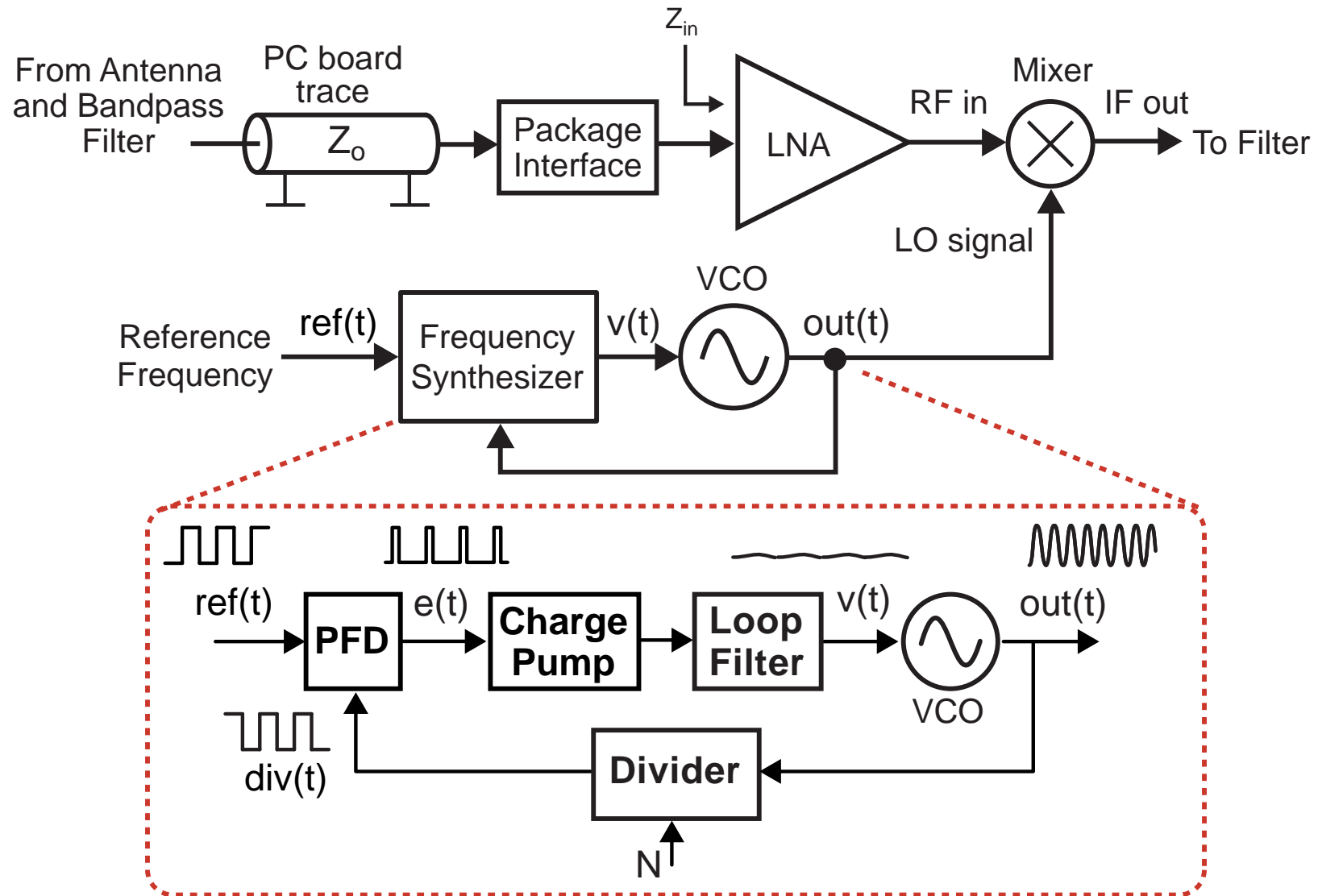
# Integer-N Frequency Synthesizers in Wireless Systems




- **Design Issues: low noise, fast settling time, low power**
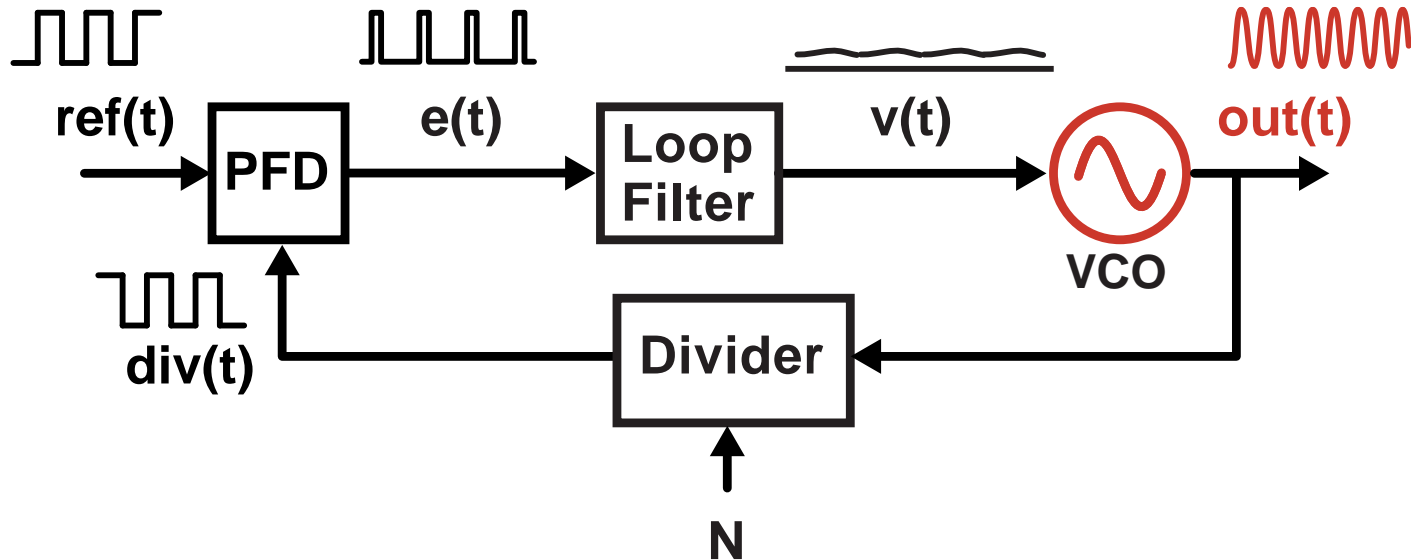
# Overview of Integer-N Frequency Synthesizer




- **VCO** → produces high frequency sine wave
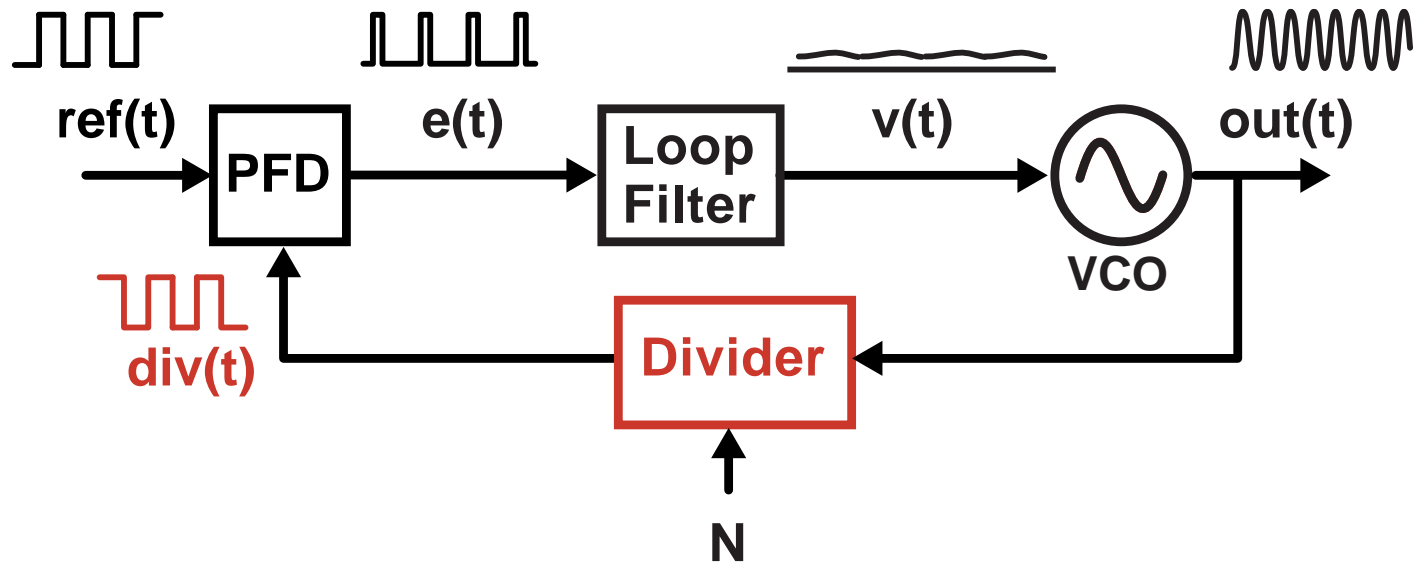
# Overview of Integer-N Frequency Synthesizer




- **VCO** → produces high frequency sine wave
- **Divider** → divides down VCO frequency
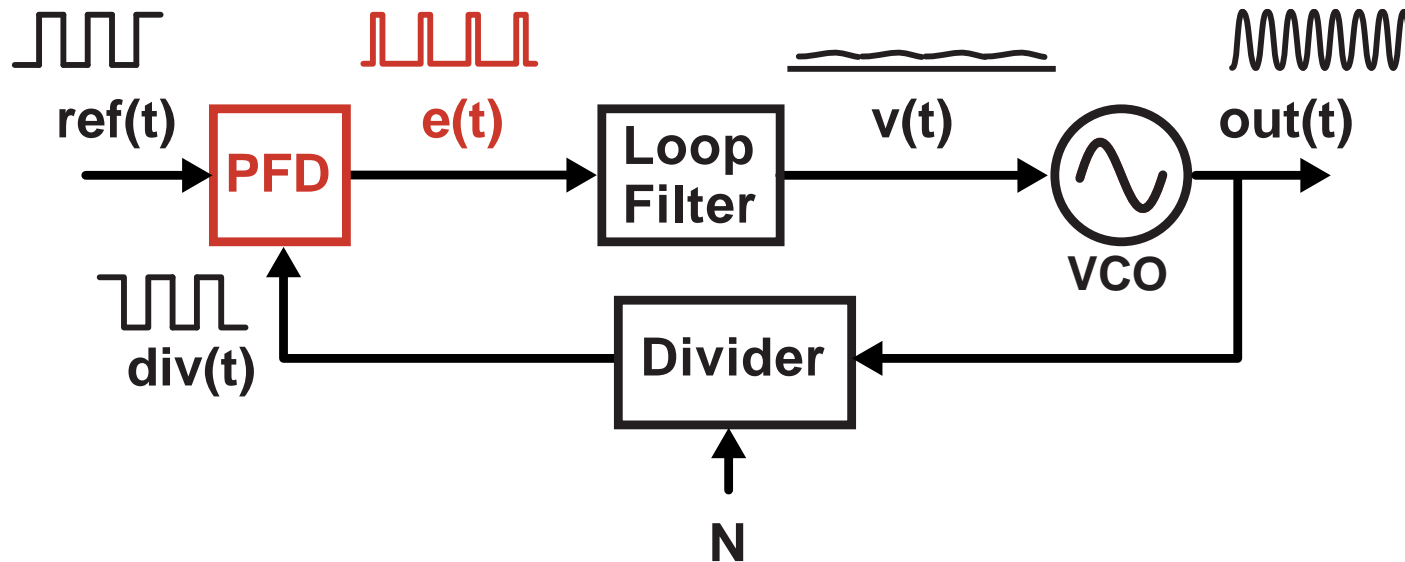
# Overview of Integer-N Frequency Synthesizer




- VCO → produces high frequency sine wave
- Divider → divides down VCO frequency
- PFD → compares phase of ref and div
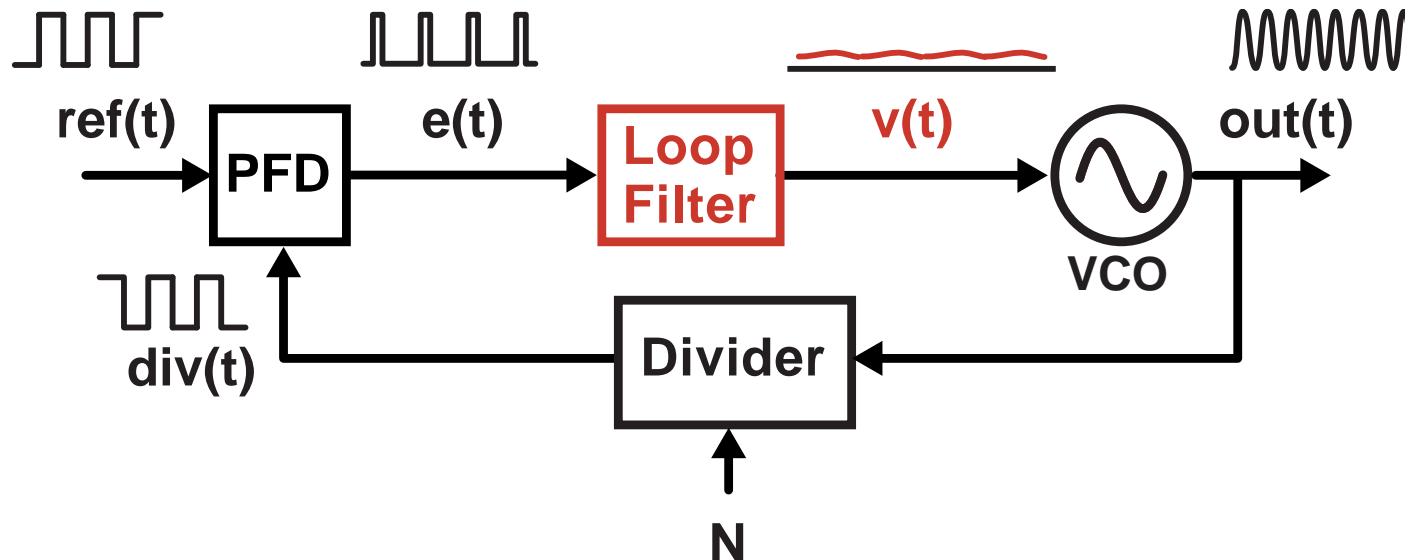
# Overview of Integer-N Frequency Synthesizer



- **VCO** → produces high frequency sine wave
- **Divider** → divides down VCO frequency
- **PFD** → compares phase of ref and div
- **Loop filter** → smooths phase error signal
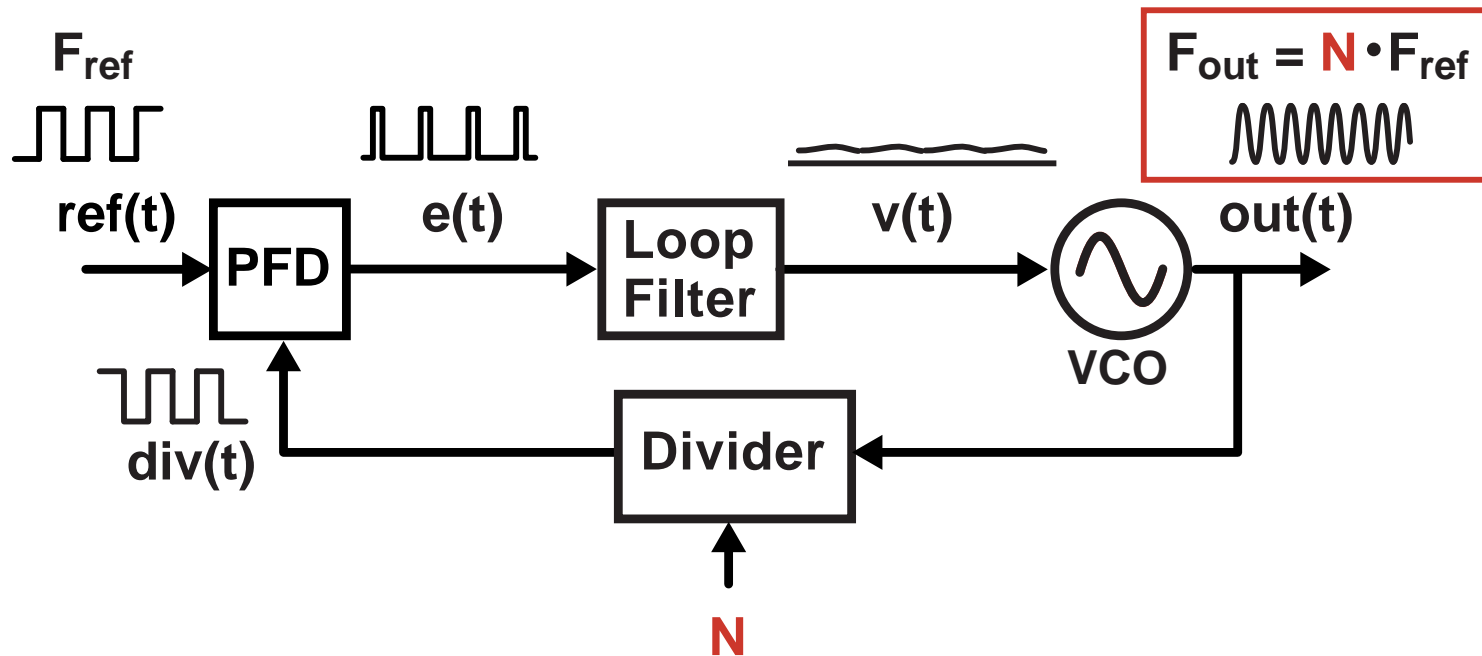
# Overview of Integer-N Frequency Synthesizer




- VCO → produces high frequency sine wave
- Divider → divides down VCO frequency
- PFD → compares phase of ref and div
- Loop filter → smooths phase error signal


VCO frequency locks to ref. frequency multiplied by N

# Popular VCO Structures

LC oscillator

 




Ring oscillator

 

- **LC Oscillator: low phase noise, large area**
- **Ring Oscillator: easy to integrate, higher phase noise**


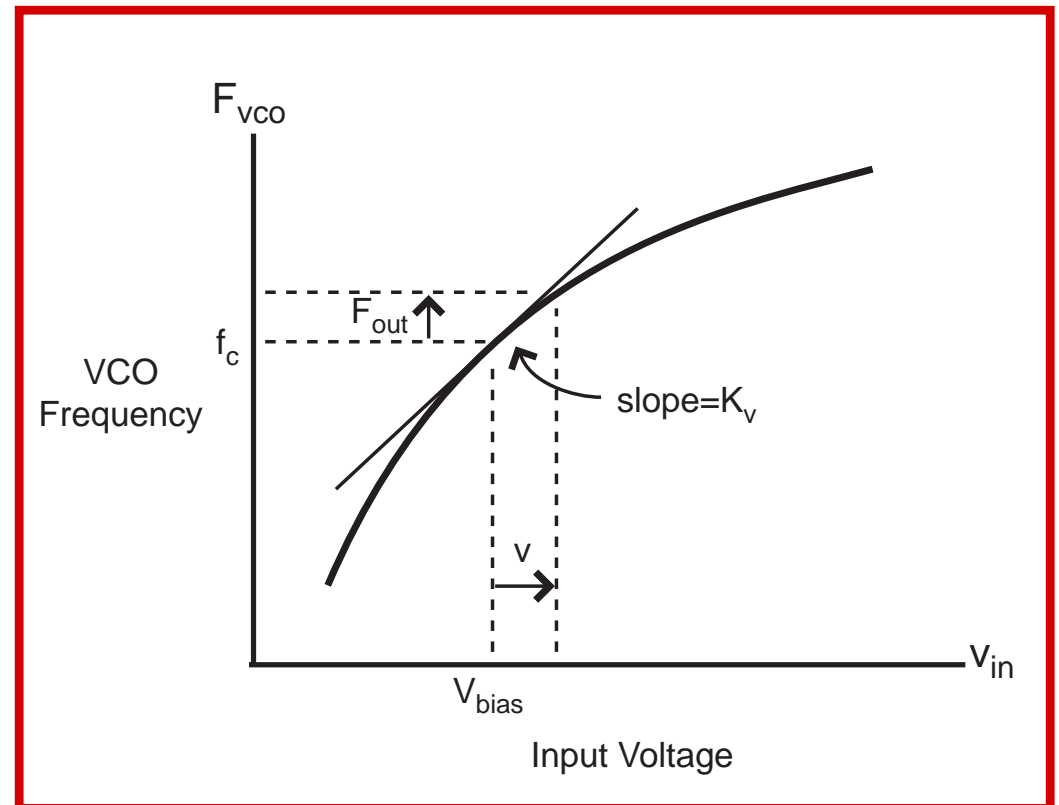  
# Model for Voltage to Frequency Mapping of VCO



$$F_{out}(t) = K_v v(t)$$

# Model for Voltage to Phase Mapping of VCO


- Time-domain frequency relationship (from previous slide)

$$F_{out}(t) = K_v v(t)$$

- Time-domain phase relationship

$$\Phi_{out}(t) = \int_{-\infty}^t 2\pi F_{out}(\tau) d\tau = \int_{-\infty}^t 2\pi K_v v(\tau) d\tau$$

 - Intuition of integral relationship between frequency and phase:




# Frequency-Domain Model for VCO

- Time-domain relationship (from previous slide)


$$\Phi_{out}(t) = \int_{-\infty}^t 2\pi K_v v(\tau) d\tau$$

- Corresponding frequency-domain model

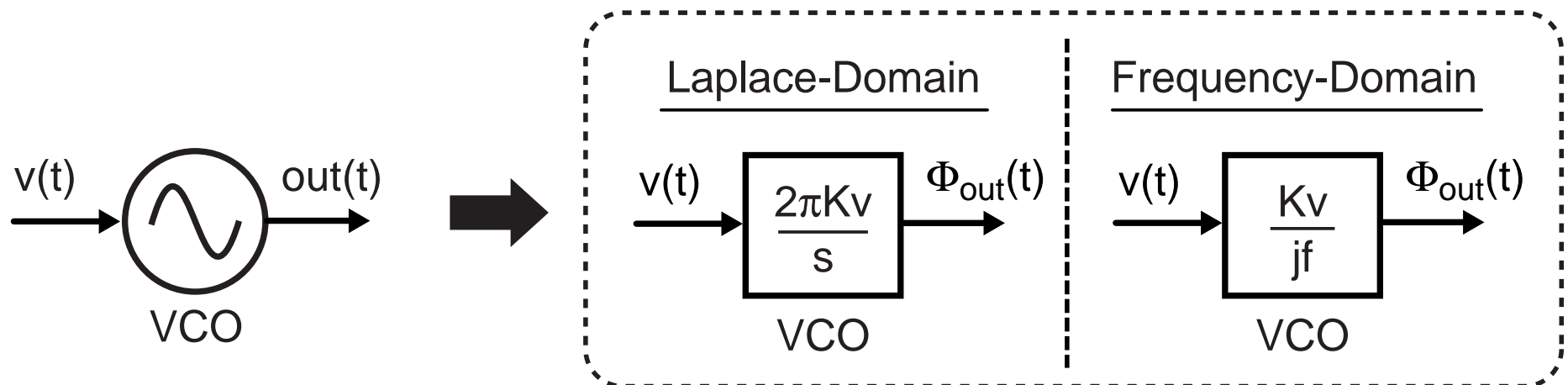

# Divider

## ■ Implementation

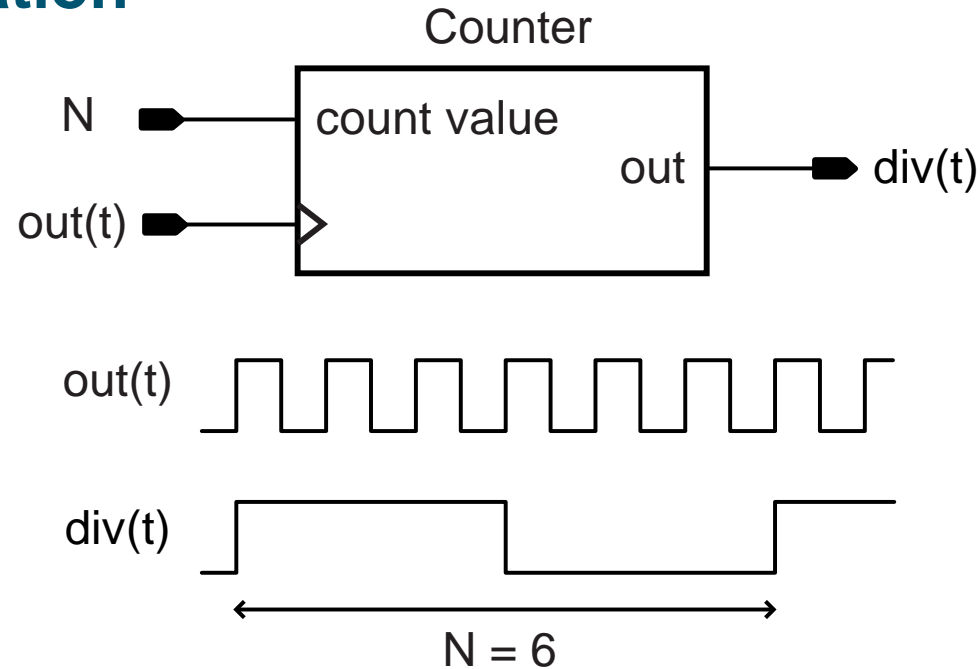

## ■ Time-domain model

### - Frequency:

$$F_{div}(t) = \frac{1}{N} F_{out}(t).$$

### - Phase:

$$\Phi_{div}(t) = \int_{-\infty}^t 2\pi \frac{1}{N} F_{out}(\tau) d\tau = \frac{1}{N} \Phi_{out}(t)$$


## Frequency-Domain Model of Divider

---

- Time-domain relationship between VCO phase and divider output phase (from previous slide)

$$\Phi_{div}(t) = \frac{1}{N} \Phi_{out}(t)$$

 - Corresponding frequency-domain model (same as Laplace-domain)





# Phase Detector (PD)

---

- XOR structure

  
- Average value of error pulses corresponds to phase error
- Loop filter extracts the average value and feeds to VCO


 
## Modeling of XOR Phase Detector

---

- Average value of pulses is extracted by loop filter
  - Look at detector output over one cycle:





- Equation:

$$\text{avg}\{e(t)\} = -1 + 2\frac{W}{T/2}$$



# Relate Pulse Width to Phase Error

- Two cases:

  



 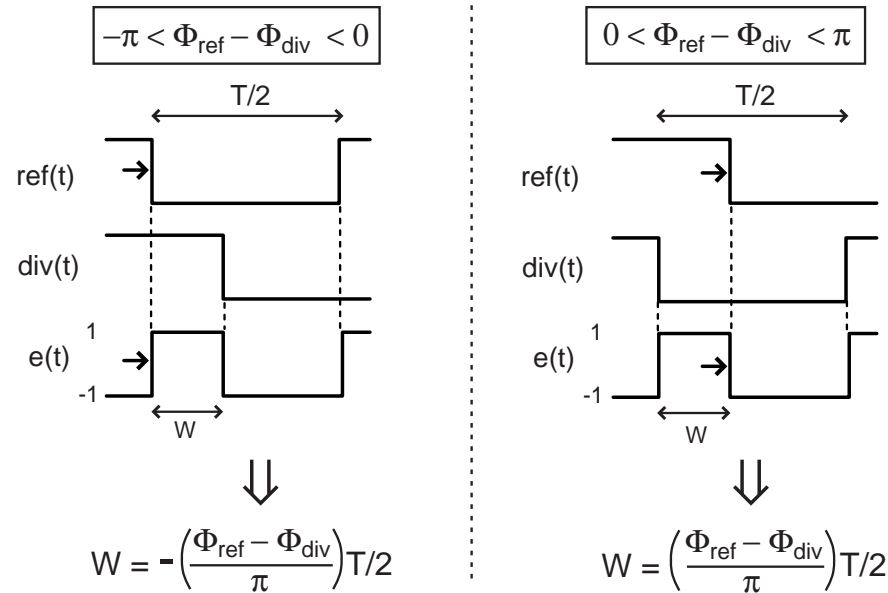
# Overall XOR Phase Detector Characteristic



 
# Frequency-Domain Model of XOR Phase Detector

- Assume phase difference confined within 0 to  $\pi$  radians
  - Phase detector characteristic looks like a constant gain element




- Corresponding frequency-domain model

 

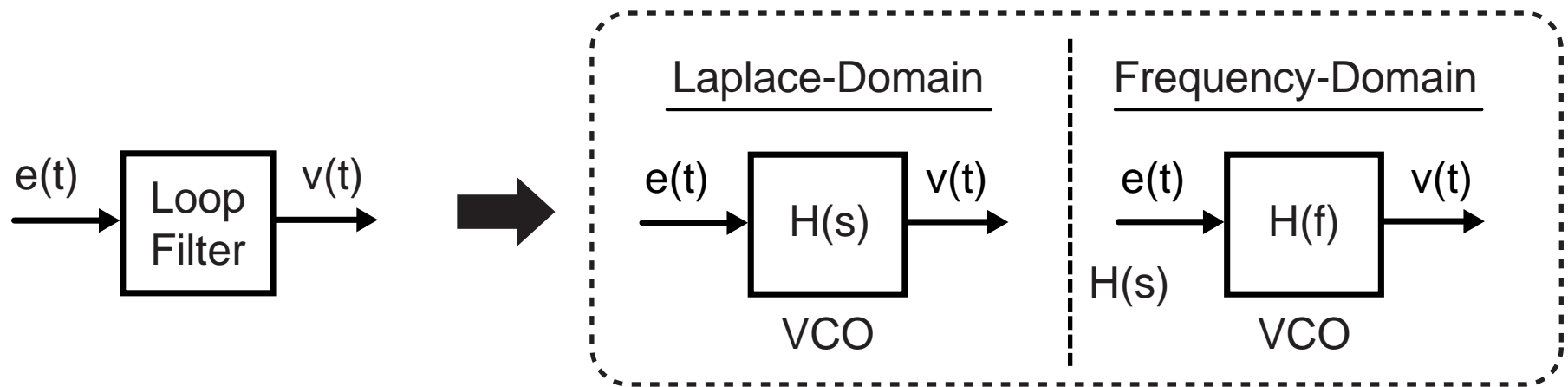
# Loop Filter

- Consists of a lowpass filter to extract average of phase detector error pulses
- Frequency-domain model



- First order example

 


$$\Rightarrow H(s) = \frac{1}{1 + sR_1C_1}$$


# Overall Linearized PLL Frequency-Domain Model

- Combine models of individual components

Laplace-Domain Model

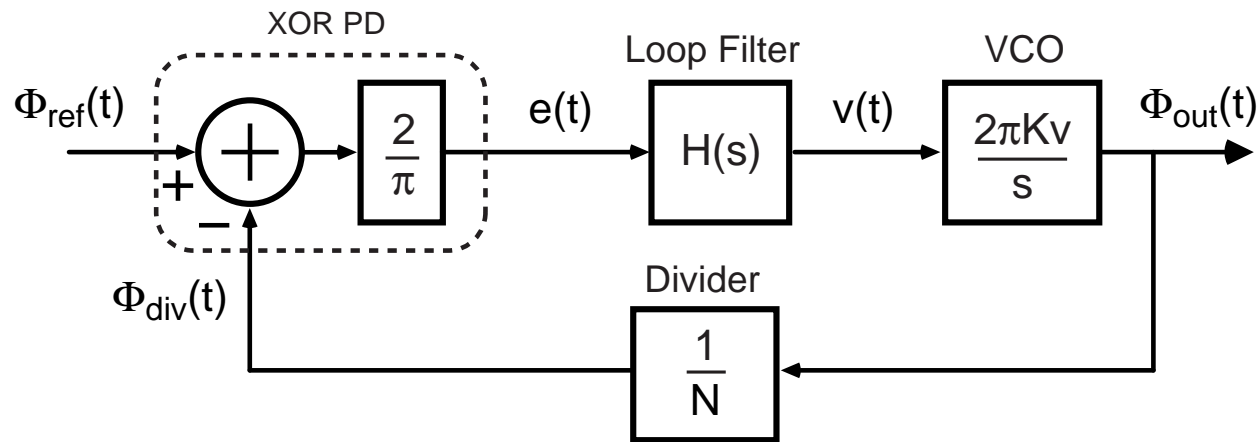


Frequency-Domain Model

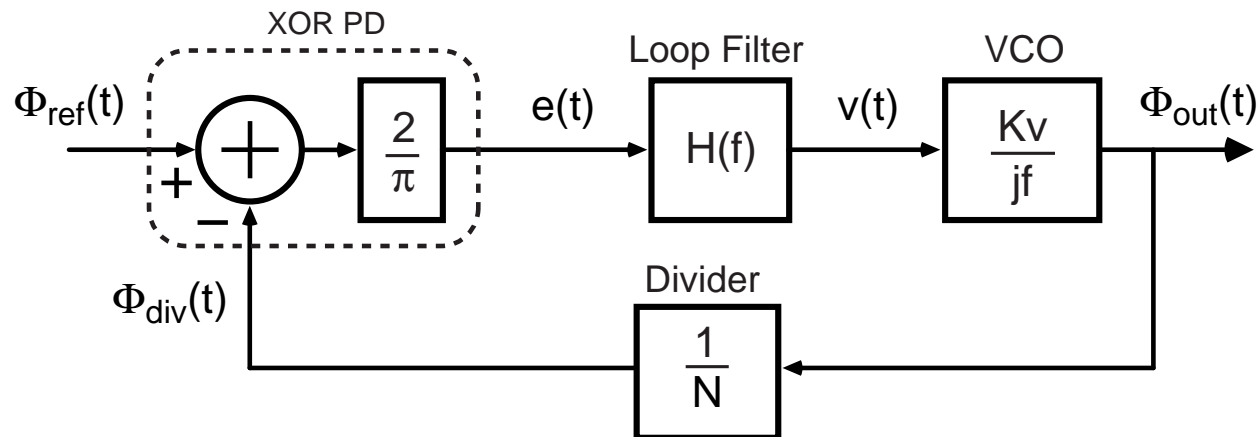

# Open Loop versus Closed Loop Response

- **Frequency-domain model**

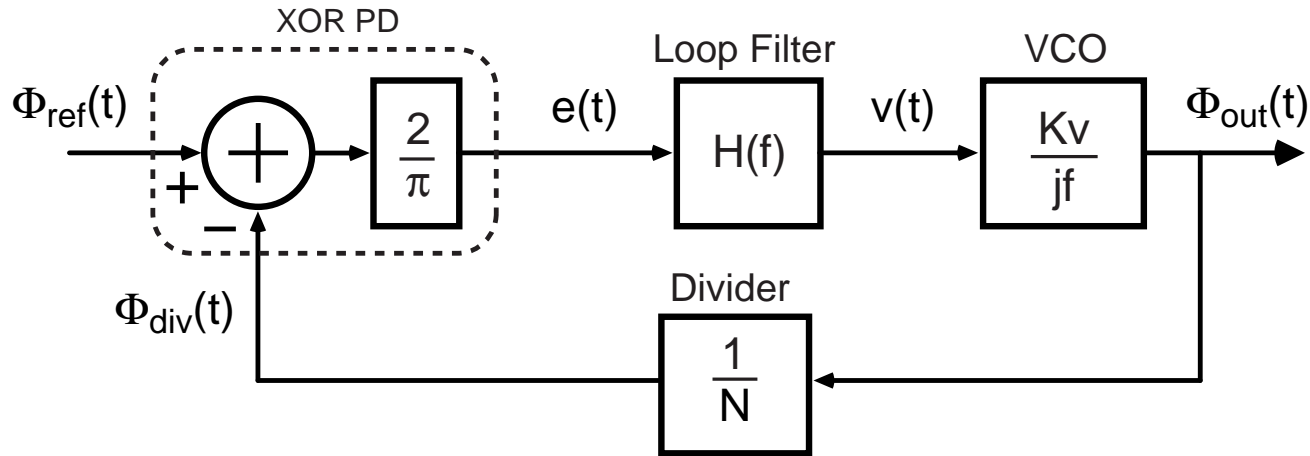

- **Define  $A(f)$  as open loop response**

$$A(f) = \frac{2}{\pi} H(f) \left( \frac{K_v}{jf} \right) \frac{1}{N}$$

- **Define  $G(f)$  as a parameterizing function (related to closed loop response)**

$$G(f) = \frac{A(f)}{1 + A(f)}$$


# Classical PLL Transfer Function Design Approach

---


1. Choose an appropriate topology for  $H(f)$ 
  - Usually chosen from a small set of possibilities
2. Choose pole/zero values for  $H(f)$  as appropriate for the required filtering of the phase detector output
  - Constraint: set pole/zero locations higher than desired PLL bandwidth to allow stable dynamics to be possible
3. Adjust the open-loop gain to achieve the required bandwidth while maintaining stability
  - Plot gain and phase bode plots of  $A(f)$
  - Use phase (or gain) margin criterion to infer stability

# Example: First Order Loop Filter

## Overall PLL block diagram

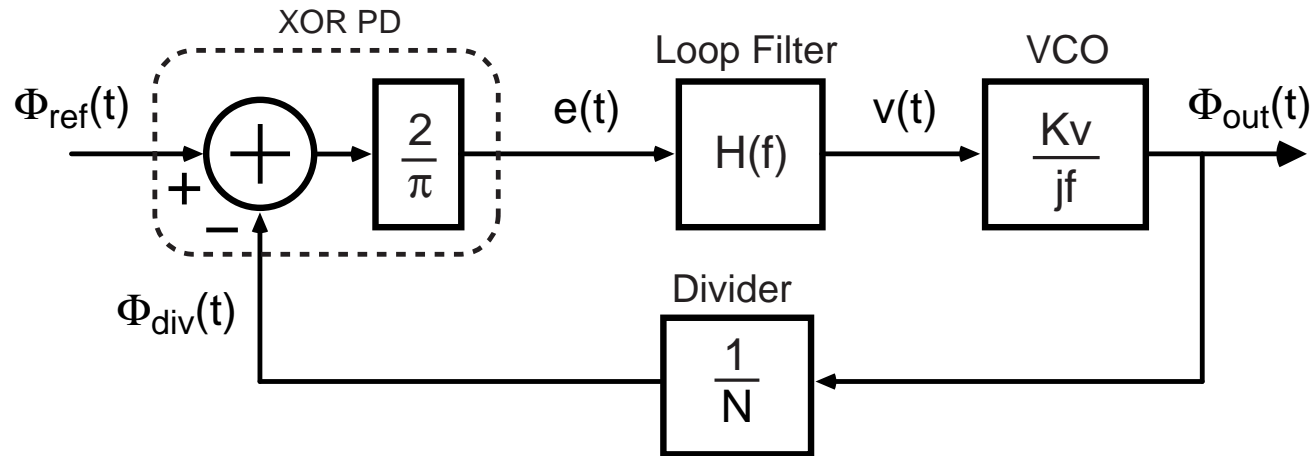


## Loop filter

 

$$\Rightarrow H(f) = \frac{1}{1 + jf/f_p}$$

 
# Closed Loop Poles Versus Open Loop Gain



- Higher open loop gain leads to an increase in  $Q$  of closed loop poles



# Corresponding Closed Loop Response

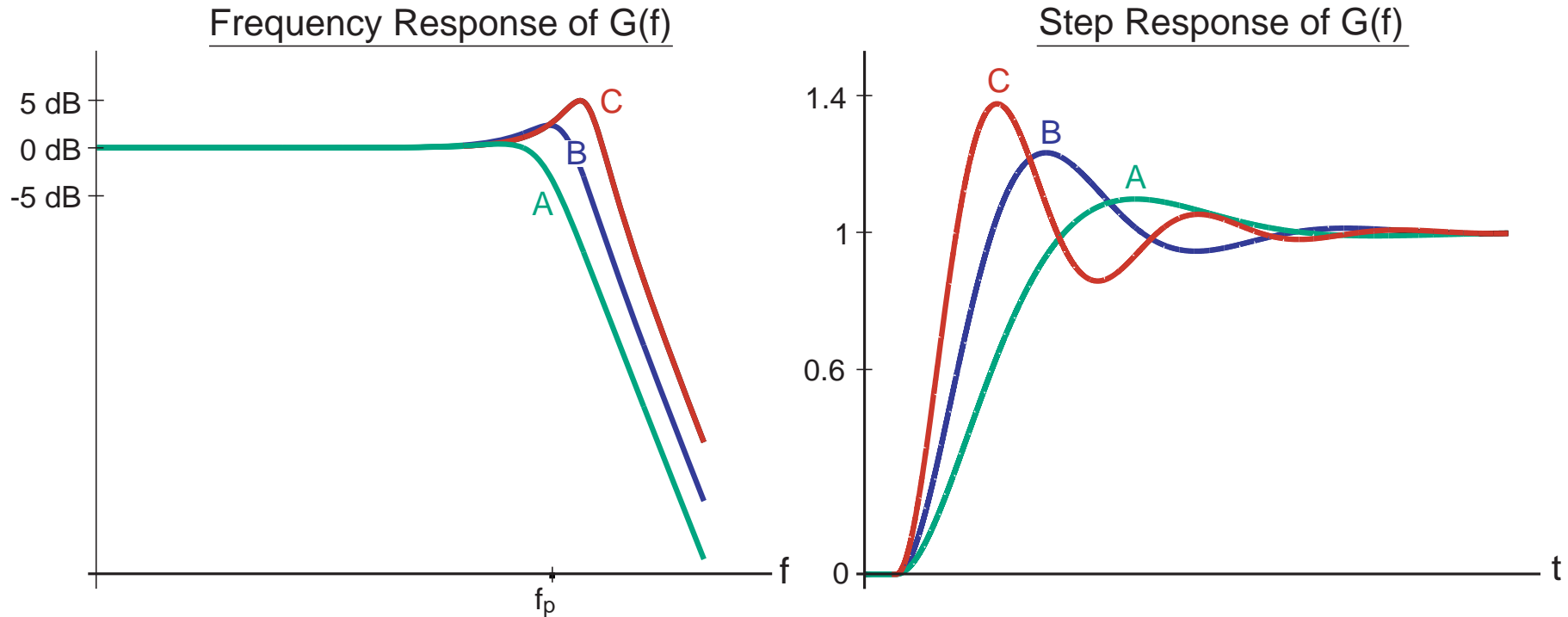


- Increase in open loop gain leads to
  - Peaking in closed loop frequency response
  - Ringing in closed loop step response
 
## The Impact of Parasitic Poles

---


- Loop filter and VCO may have additional parasitic poles and zeros due to their circuit implementation
- We can model such parasitics by including them in the loop filter transfer function
- Example: add two parasitic poles to first order filter




$$\Rightarrow H(f) = \left( \frac{1}{1 + jf/f_1} \right) \left( \frac{1}{1 + jf/f_2} \right) \left( \frac{1}{1 + jf/f_3} \right)$$

# Closed Loop Poles Versus Open Loop Gain



Evaluation of Phase Margin

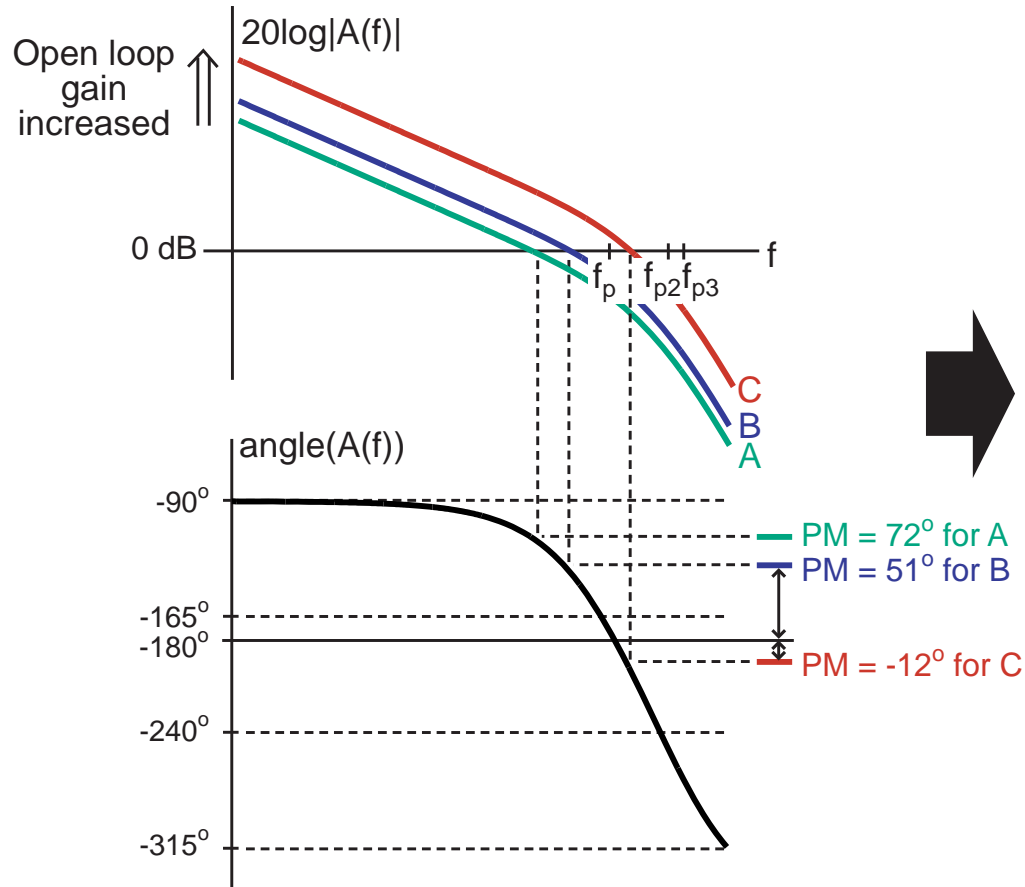

Closed Loop Pole Locations of  $G(f)$

 


# Corresponding Closed Loop Response

  

- Increase in open loop gain now eventually leads to instability
  - Large peaking in closed loop frequency response
  - Increasing amplitude in closed loop step response

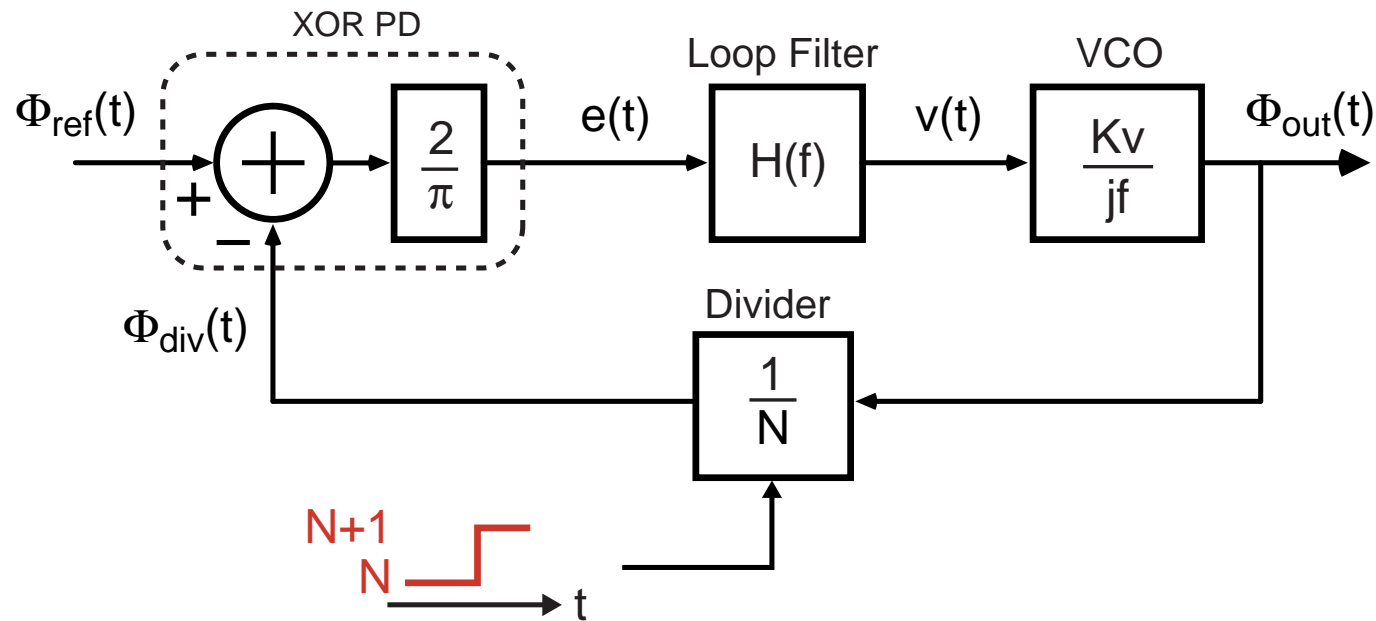
# Response of PLL to Divide Value Changes



- Change in output frequency achieved by changing the divide value
- Classical approach provides no direct model of impact of divide value variations
  - Treat divide value variation as a perturbation to a linear system
    - PLL responds according to its closed loop response

# Response of an Actual PLL to Divide Value Change


- Example: Change divide value by one

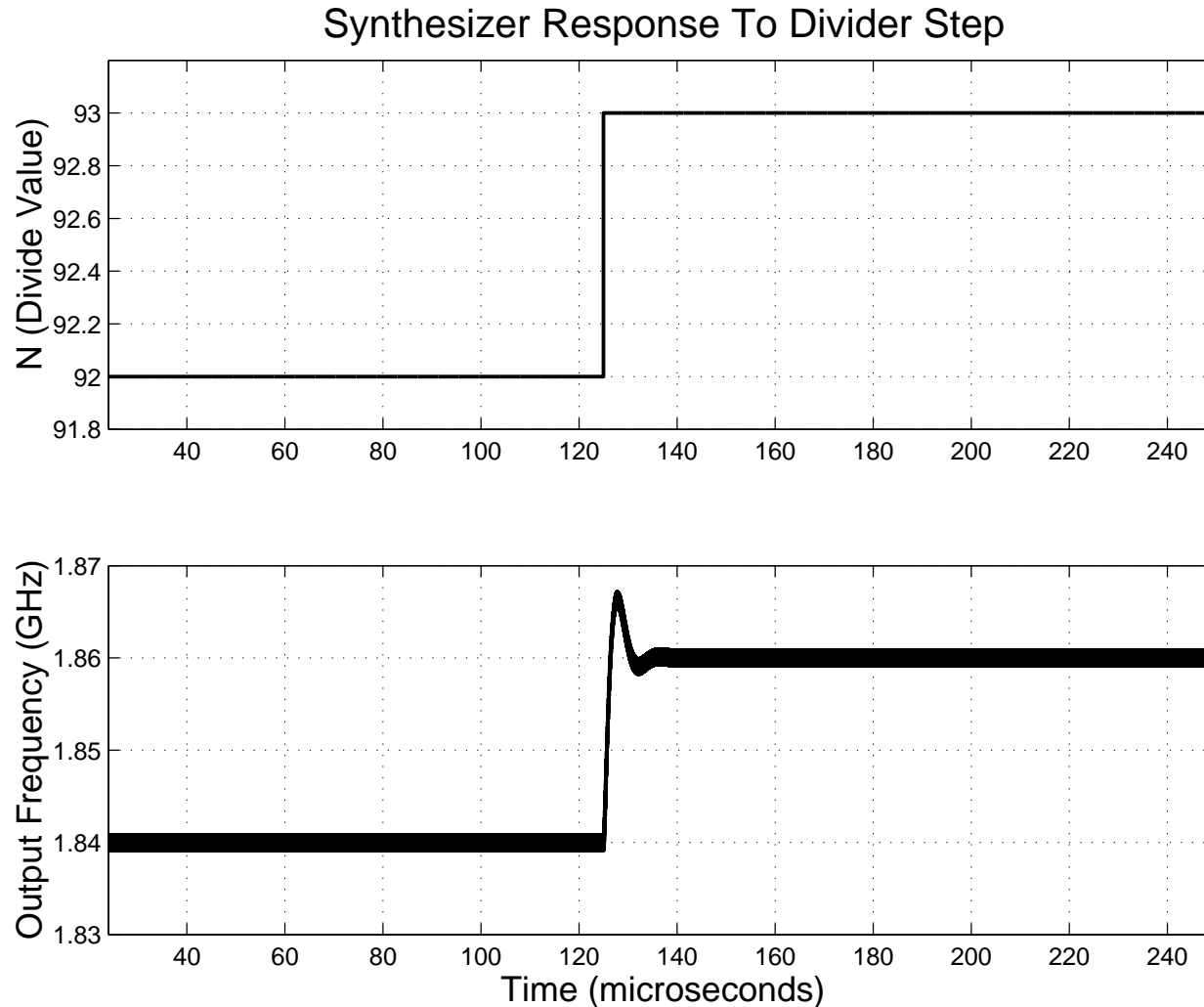

- PLL responds according to closed loop response!

 
# What Happens with Large Divide Value Variations?

- PLL temporarily loses frequency lock (cycle slipping occurs)



- Why does this happen?

## Recall Phase Detector Characteristic

 


- To simplify modeling, we assumed that we always operated in a confined phase range (0 to  $\pi$ )
  - Led to a simple PD model
- Large perturbations knock us out of that confined phase range
  - PD behavior varies depending on the phase range it happens to be in



 
# Cycle Slipping

- Consider the case where there is a frequency offset between divider output and reference
  - We know that phase difference will accumulate




 - Resulting ramp in phase causes PD characteristic to be swept across its different regions (cycle slipping)



 
# Impact of Cycle Slipping

- Loop filter averages out phase detector output
- Severe cycle slipping causes phase detector to alternate between regions very quickly
  - Average value of XOR characteristic can be close to zero
  - PLL frequency oscillates according to cycle slipping
  - In severe cases, PLL will not re-lock
    - PLL has finite frequency lock-in range!


 
## Back to PLL Response Shown Previously



- PLL output frequency indeed oscillates
  - Eventually locks when frequency difference is small enough



- How do we extend the frequency lock-in range?


# Phase Frequency Detectors (PFD)

## ■ Example: Tristate PFD

  
 
## Tristate PFD Characteristic


- Calculate using similar approach as used for XOR phase detector



- Note that phase error characteristic is asymmetric about zero phase
  - Key attribute for enabling frequency detection


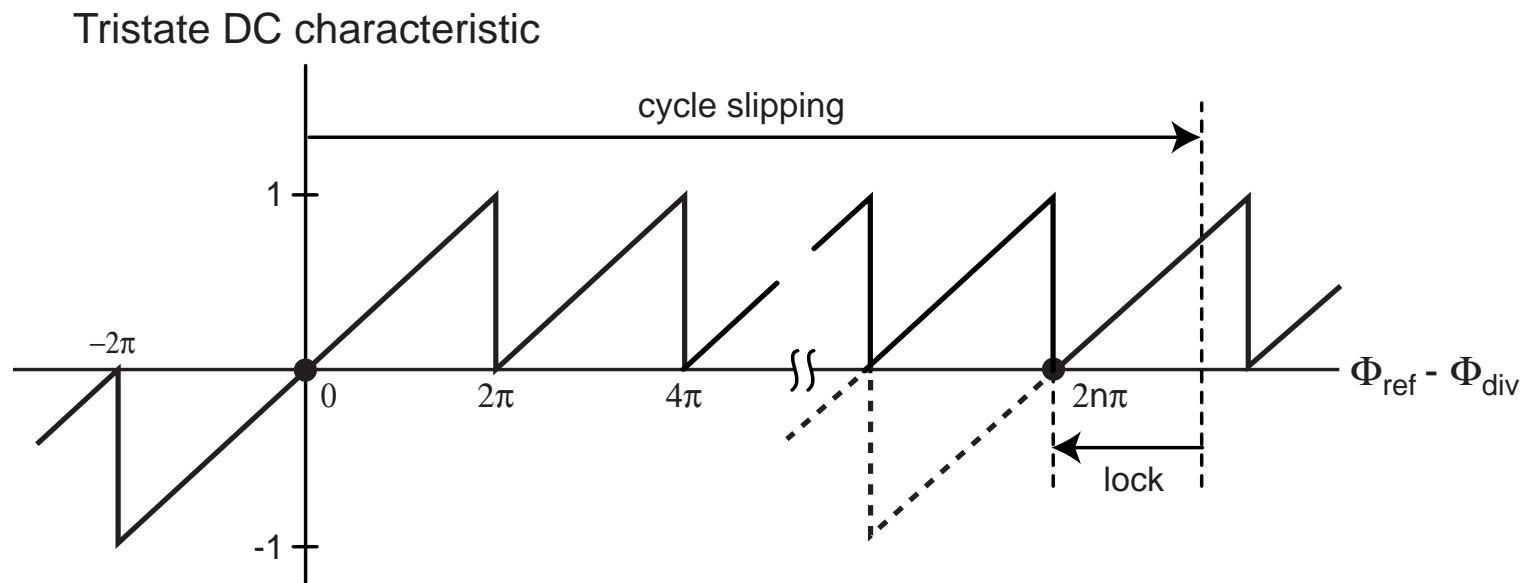
# PFD Enables PLL to Always Regain Frequency Lock

- Asymmetric phase error characteristic allows positive frequency differences to be distinguished from negative frequency differences
  - Average value is now positive or negative according to sign of frequency offset
  - PLL will always relock




# Another PFD Structure

## ■ XOR-based PFD

 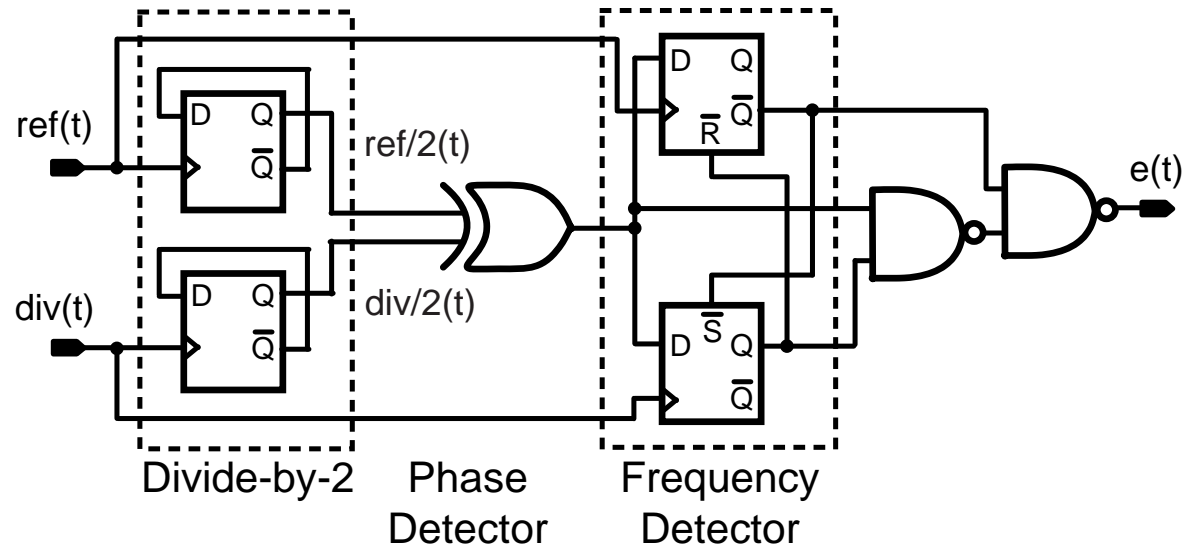
 
# XOR-based PFD Characteristic

- Calculate using similar approach as used for XOR phase detector




- Phase error characteristic asymmetric about zero phase
  - Average value of phase error is positive or negative during cycle slipping depending on sign of frequency error



 
# Linearized PLL Model With PFD Structures

- Assume that when PLL in lock, phase variations are within the linear range of PFD
  - Simulate impact of cycle slipping if desired (do not include its effect in model)
- Same frequency-domain PLL model as before, but PFD gain depends on topology used



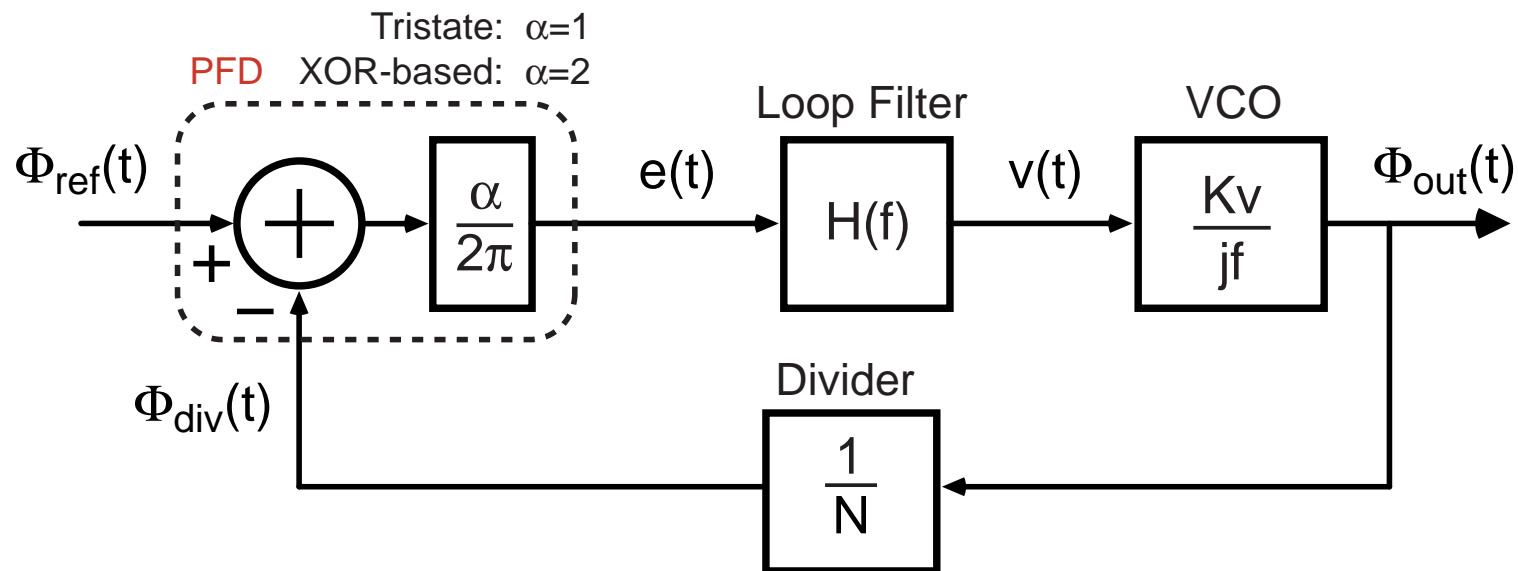
# Type I versus Type II PLL Implementations

- **Type I: one integrator in PLL open loop transfer function**
  - VCO adds on integrator
  - Loop filter,  $H(f)$ , has no integrators
- **Type II: two integrators in PLL open loop transfer function**
  - Loop filter,  $H(f)$ , has one integrator



 
# VCO Input Range Issue for Type I PLL Implementations

- DC output range of gain block versus integrator



- Issue: DC gain of loop filter often small and PFD output range is limited

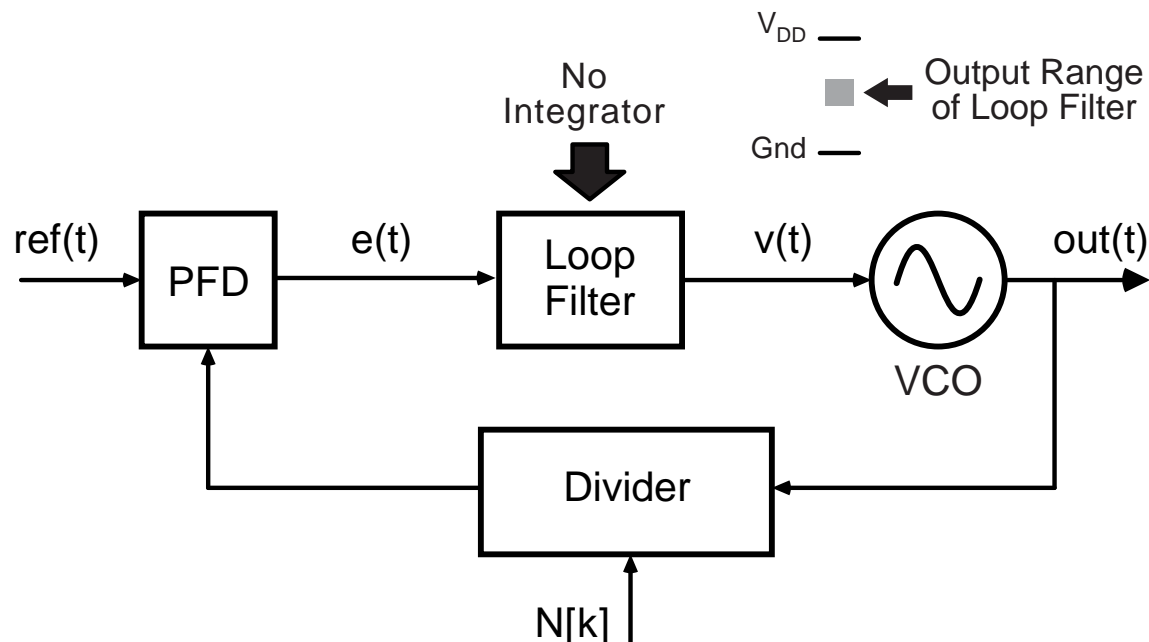- Loop filter output fails to cover full input range of VCO




# Options for Achieving Full Range Span of VCO

## ■ Type I

- Add a D/A converter to provide coarse tuning
  - Adds power and complexity
  - Steady-state phase error inconsistently set
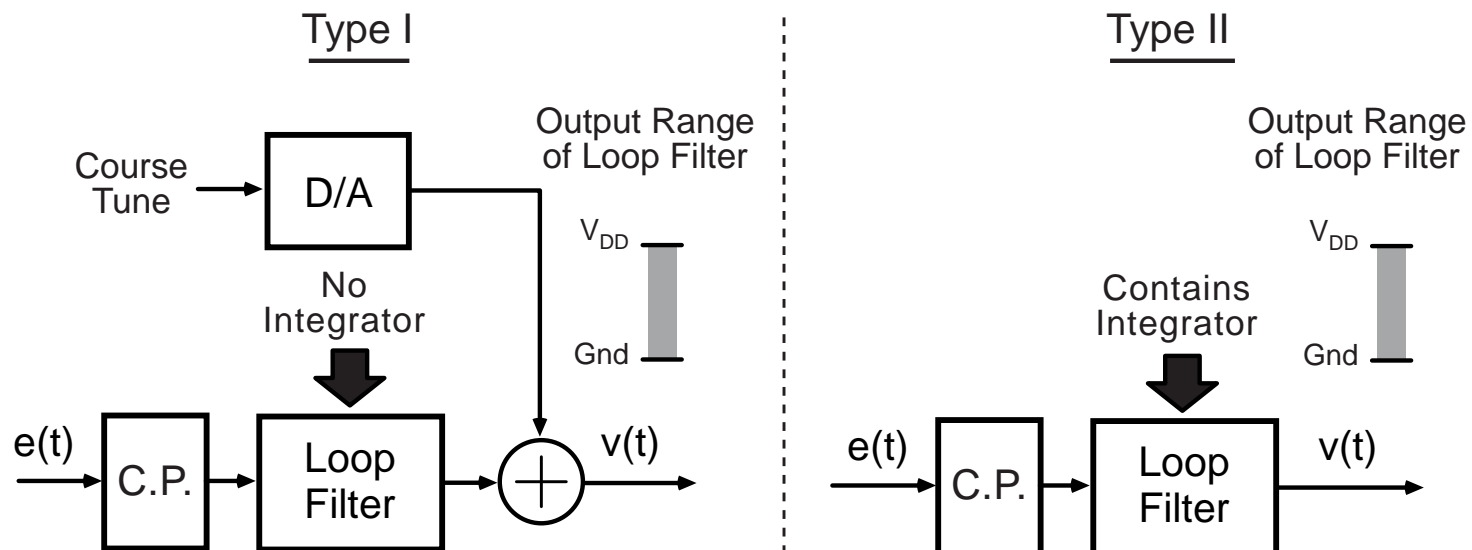
## ■ Type II


- Integrator automatically provides DC level shifting
  - Low power and simple implementation
  - Steady-state phase error always set to zero


 
# A Common Loop Filter for Type II PLL Implementation


---

- Use a charge pump to create the integrator
  - Current onto a capacitor forms integrator
  - Add extra pole/zero using resistor and capacitor
- Gain of loop filter can be adjusted according to the value of the charge pump current
- Example: lead/lag network




# Charge Pump Implementations

- Switch currents in and out:

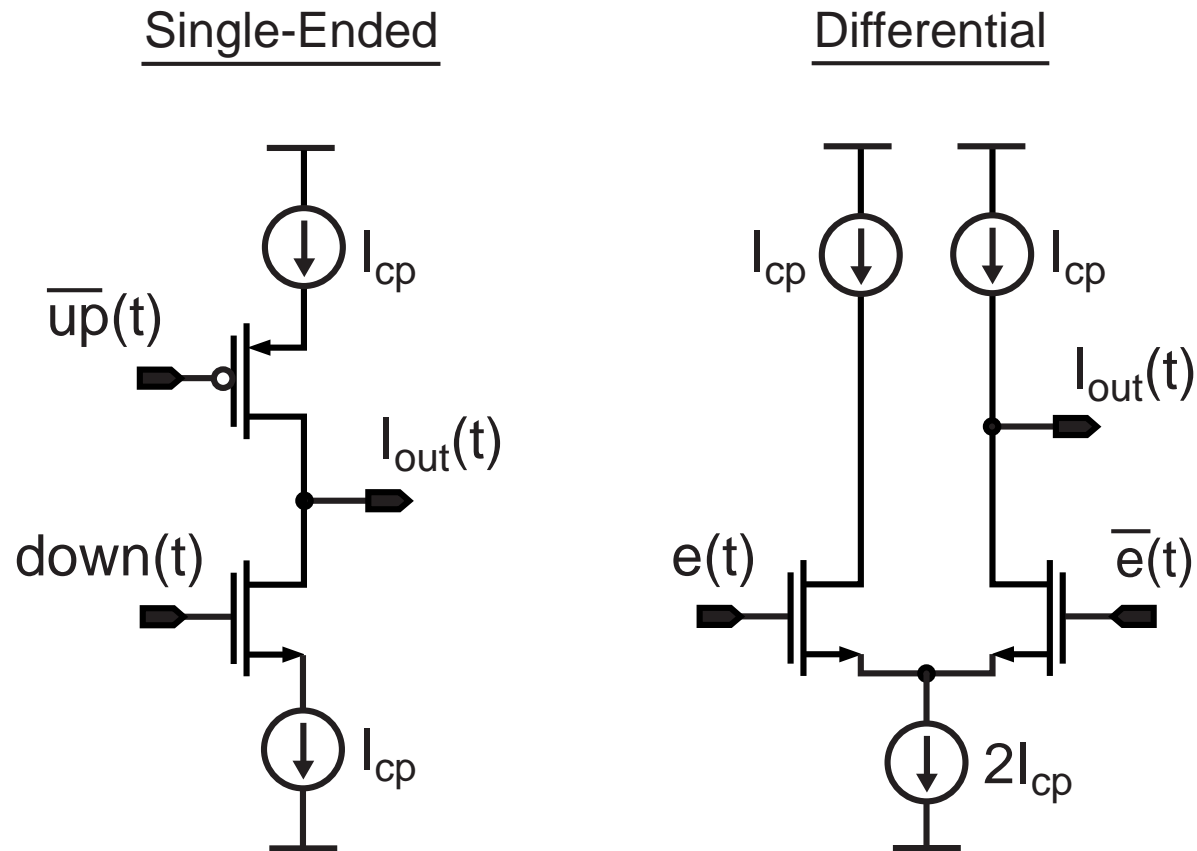
 
# Modeling of Loop Filter/Charge Pump

- Charge pump is gain element
- Loop filter forms transfer function




- Example: lead/lag network from previous slide

$$H(f) = \left( \frac{1}{sC_{sum}} \right) \frac{1 + jf/f_z}{1 + jf/f_p}$$

$$C_{sum} = C_1 + C_2, \quad f_z = \frac{1}{2\pi R_1 C_2}, \quad f_p = \frac{C_1 + C_2}{2\pi R_1 C_1 C_2}$$

# PLL Design with Lead/Lag Filter

## Overall PLL block diagram

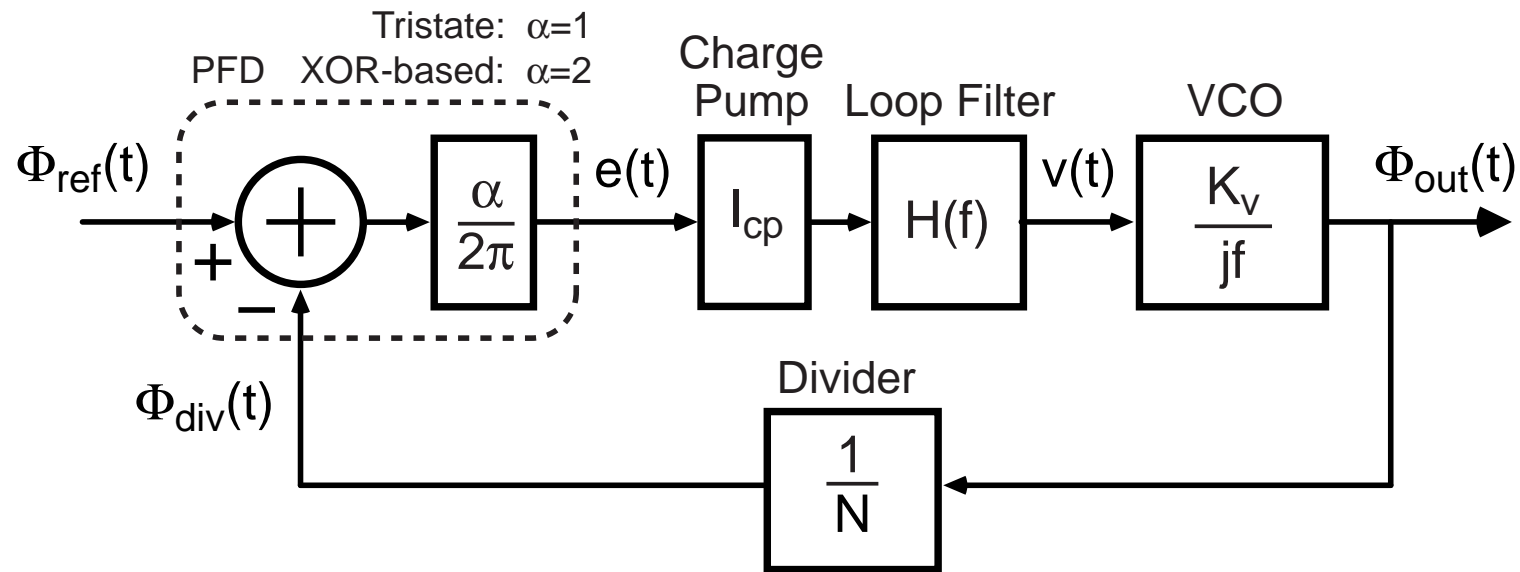


## Loop filter

$$H(f) = \left( \frac{1}{sC_{sum}} \right) \frac{1 + jf/f_z}{1 + jf/f_p}$$

- Set open loop gain to achieve adequate phase margin
  - Set  $f_z$  lower than and  $f_p$  higher than desired PLL bandwidth



 
# Closed Loop Poles Versus Open Loop Gain



- Open loop gain cannot be too low or too high if reasonable phase margin is desired
 
## Impact of Parasitics When Lead/Lag Filter Used


- We can again model impact of parasitics by including them in loop filter transfer function



- Example: include two parasitic poles with the lead/lag transfer function



$$H(f) = \left( \frac{1}{sC_{sum}} \right) \frac{1 + jf/f_z}{1 + jf/f_p} \left( \frac{1}{1 + jf/f_{p2}} \right) \left( \frac{1}{1 + jf/f_{p3}} \right)$$
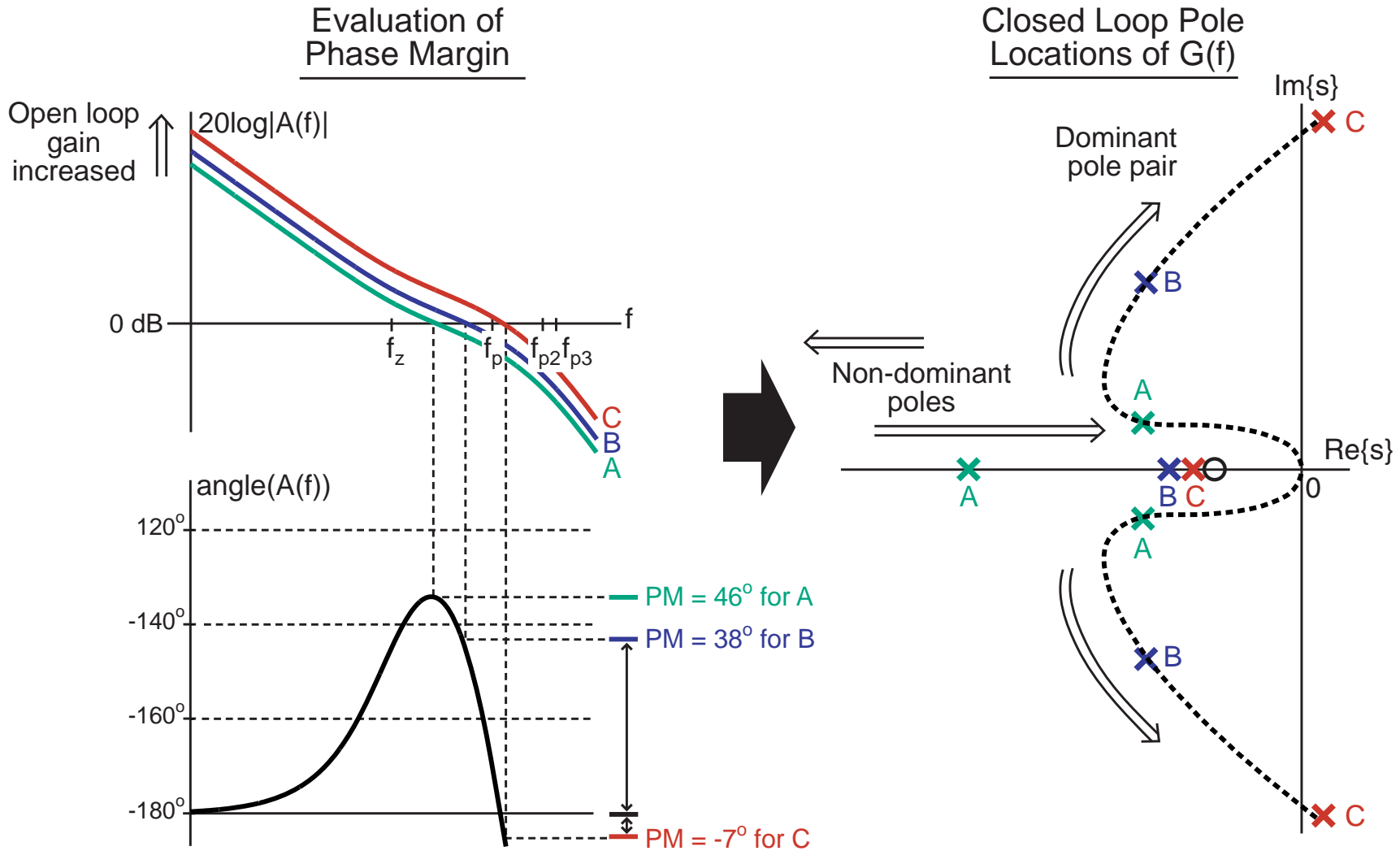
# Closed Loop Poles Versus Open Loop Gain



- Closed loop response becomes unstable if open loop gain is too high
  
# Negative Issues For Type II PLL Implementations



- **Parasitic pole/zero pair causes**
  - **Peaking in the closed loop frequency response**
    - A big issue for CDR systems, but not too bad for wireless
  - **Extended settling time due to parasitic “tail” response**
    - Bad for wireless systems demanding fast settling time